

place in scan matrix? would need 3-4 wires to UPPER board instead of 2!
 No. UOL+ or UOL- can either be connected to GPIOs
 or drive two FETs that sit in the keyboard matrix
 in any case it is sufficient to connect GPIO-UOL+ and UOL- to two pins on the B2B connector

Buttons

TITLE: GTA04b7-jr-first-beautify


Document Number:

REU:
v2b

Date: 09.09.15 02:12

Sheet: 1/35

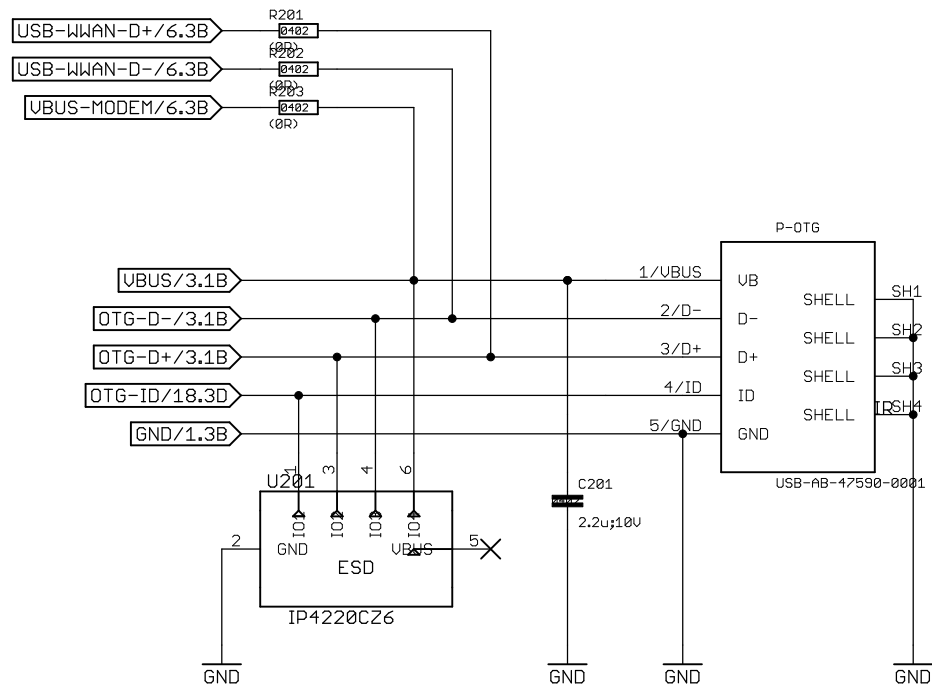can be used to test/operate the modem through the OTG port (w/o UPPER PCB)



OTG


TITLE: GTA04b7-jr-first-beautify

Document Number:

REU:
v2b

Date: 09.09.15 02:12

Sheet: 2/35

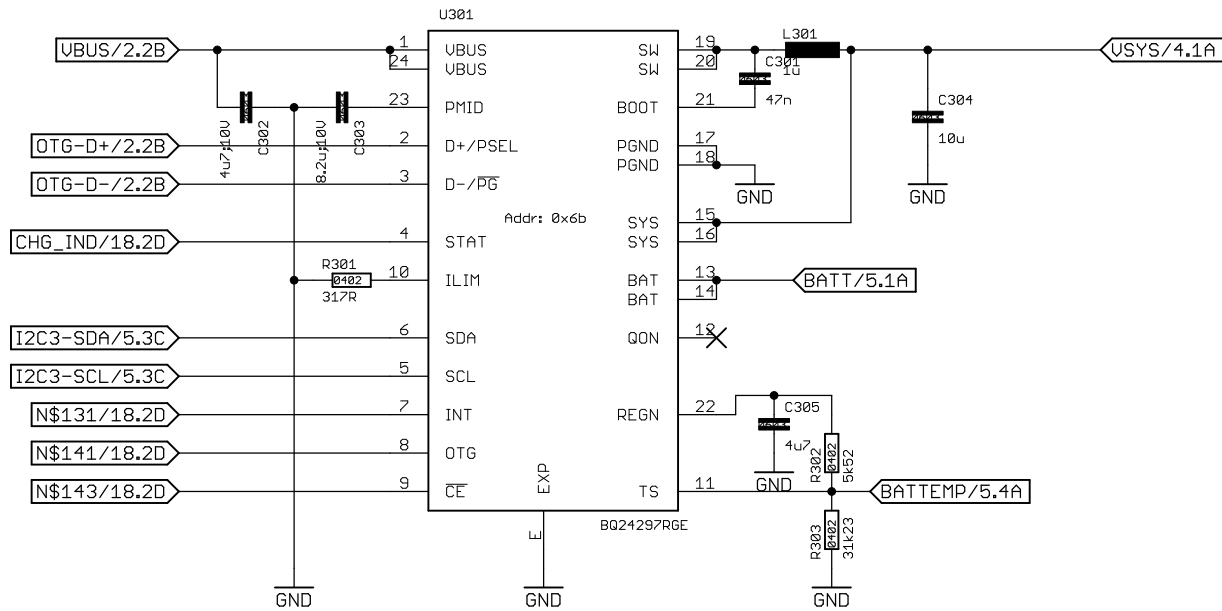

Charger/OTG-Booster


TITLE: GTA04b7-jr-first-beautify

Document Number:

REV:
v2b

Date: 09.09.15 02:12

Sheet: 3/35

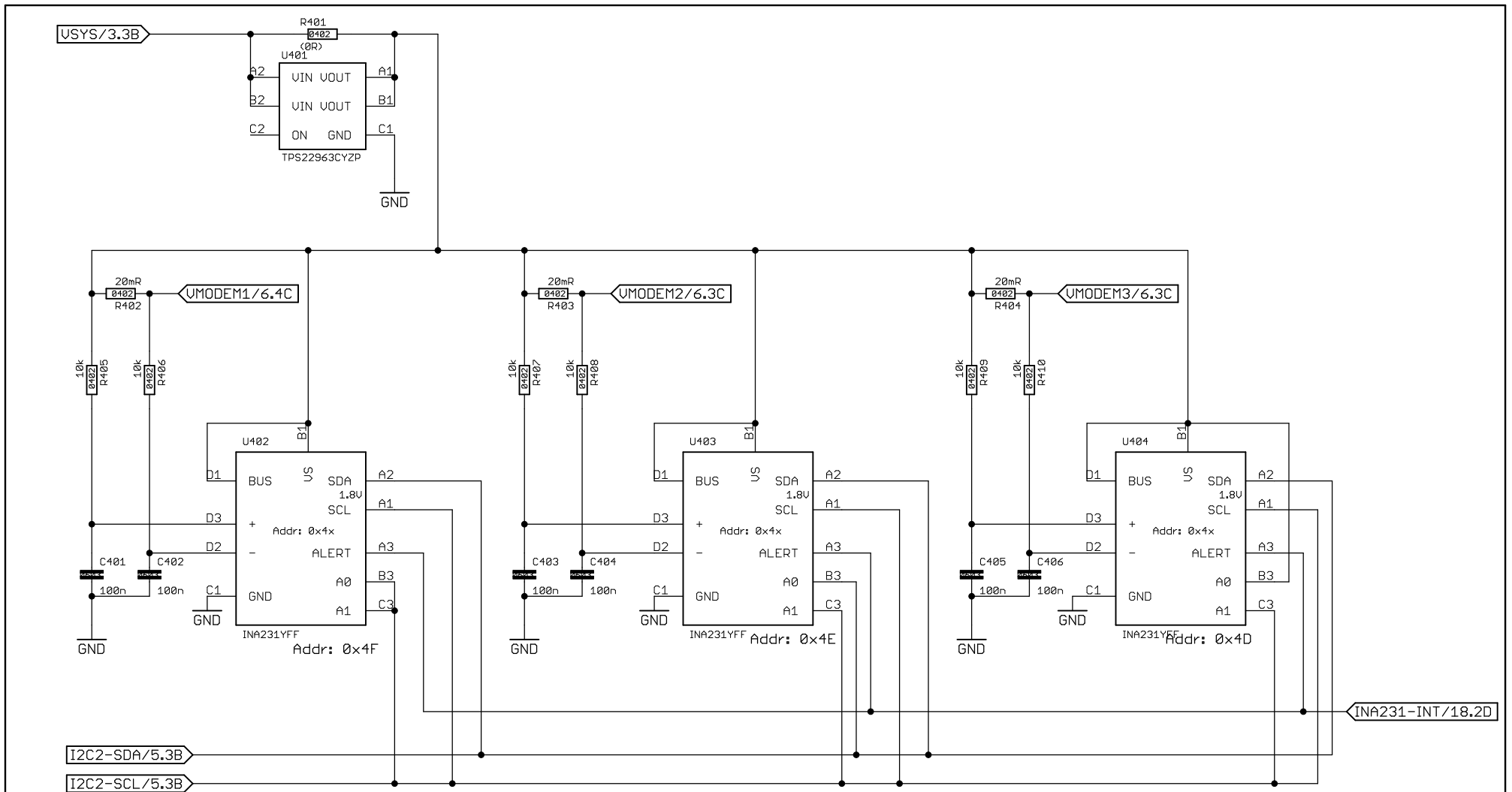

Modem Power


TITLE: GTA04b7-jr-first-beautify

Document Number:

REU:
v2b

Date: 09.09.15 02:12


Sheet: 4/35

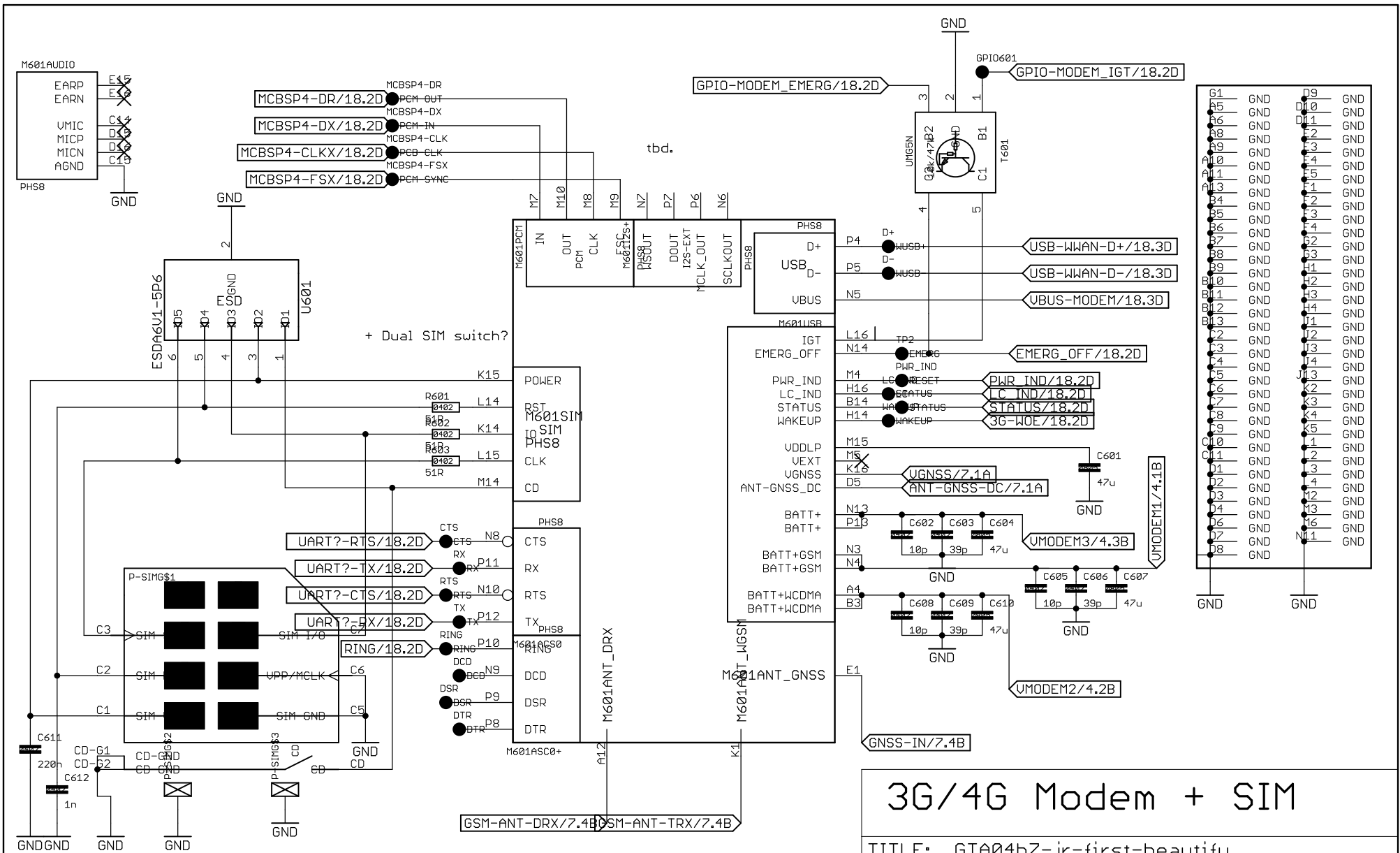



3G/4G Modem + SIM

TITLE: GTA04b7-jr-first-beautify	
Document Number:	REU: v2b
Date: 09.09.15 02:12	Sheet: 6/35

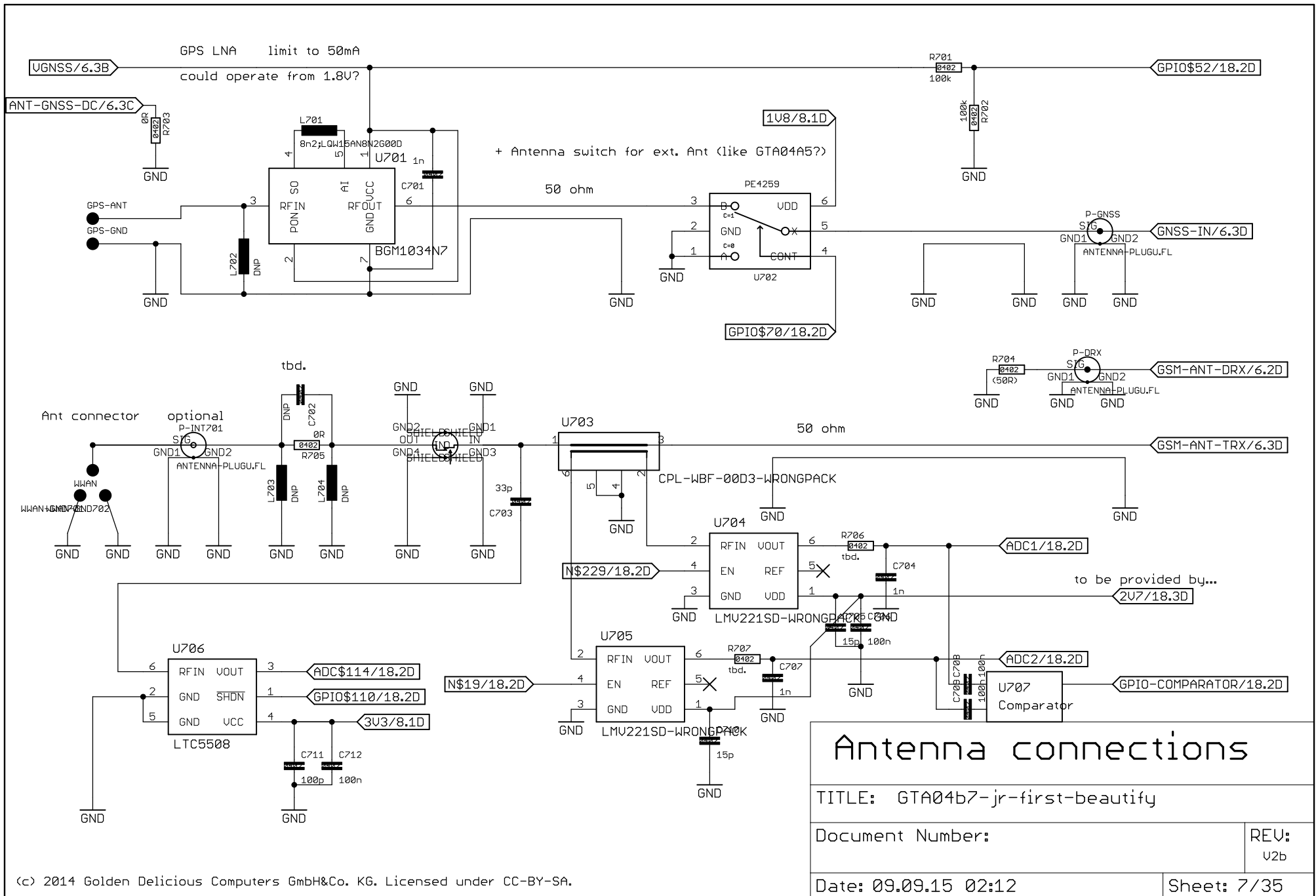
Can we connect UART in parallel to Bluetooth UART (i.e. if BT is disabled we can unbrick the Modem?)



Antenna connections	
TITLE: GTA04b7-jr-first-beautify	
Document Number:	REU: v2b
Date: 09.09.15 02:12	Sheet: 7/35

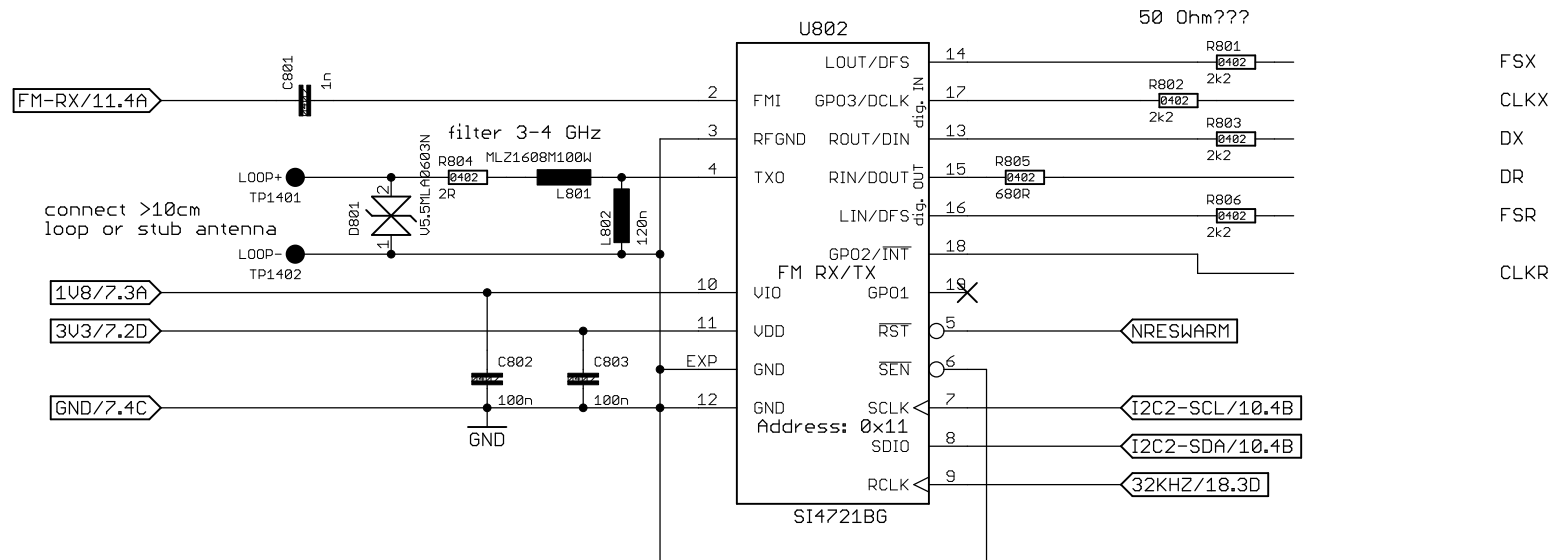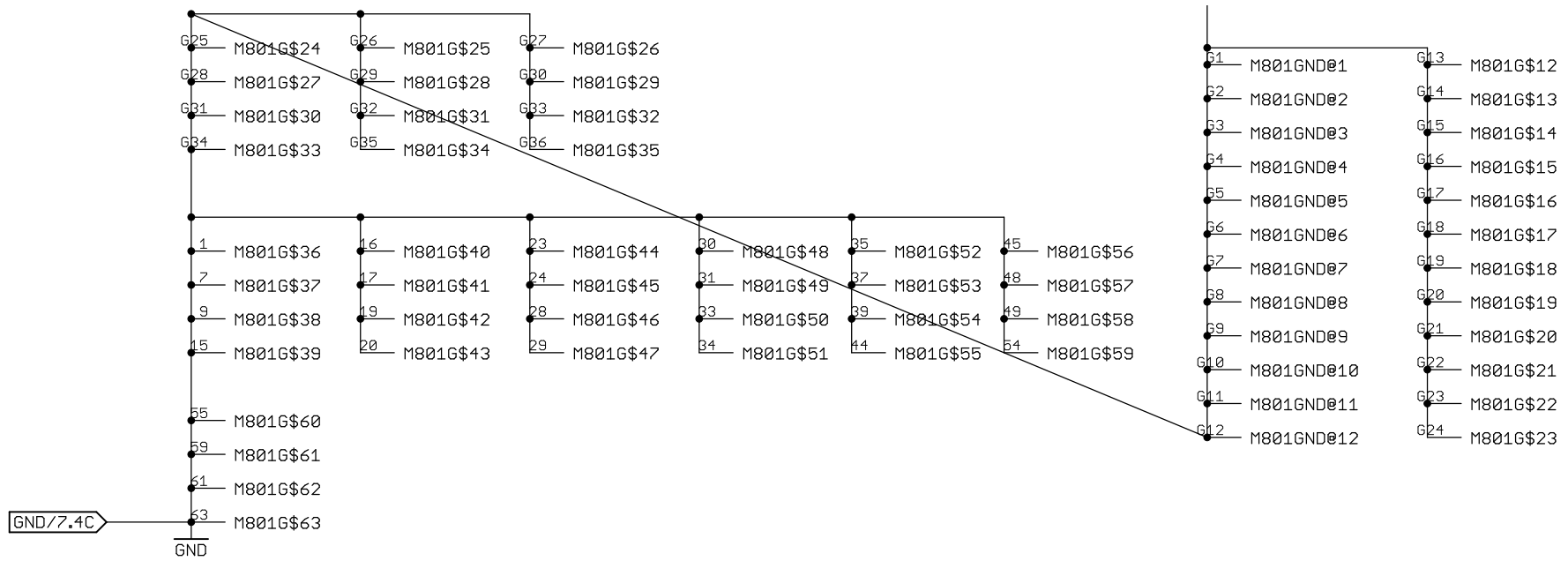

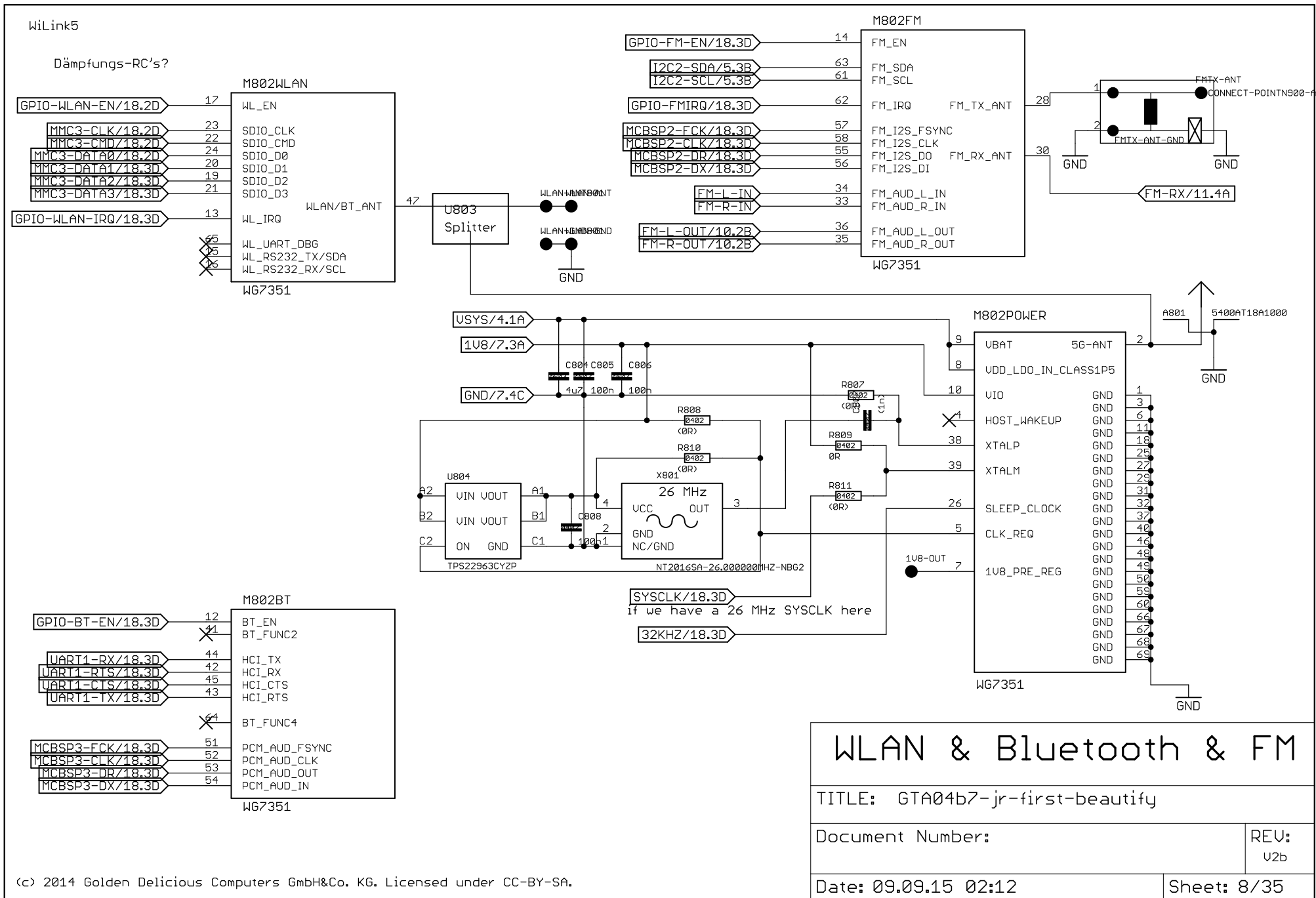Si4705 is pin compatible (mostly) but RX-only



WLAN & Bluetooth & FM

TITLE: GTA04b7-jr-first-beautify



Document Number:

REV:
v2b

Date: 09.09.15 02:12




Sheet: 8/35

WiLink8

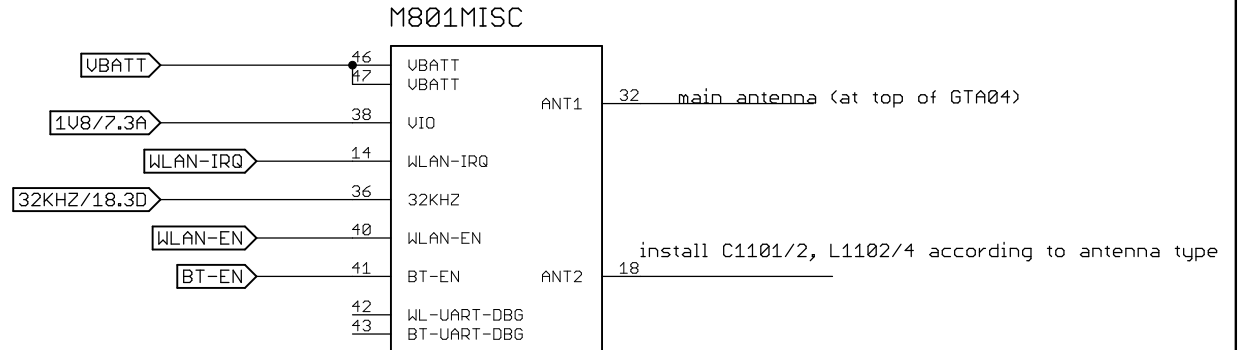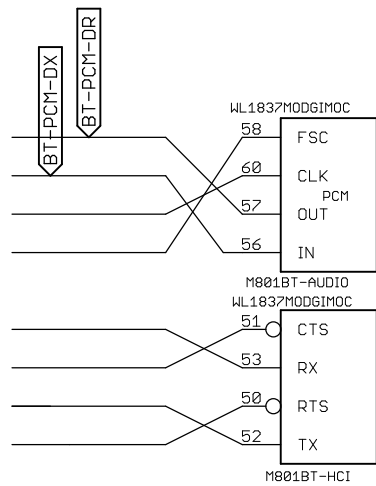

WL1837MODGIMOC

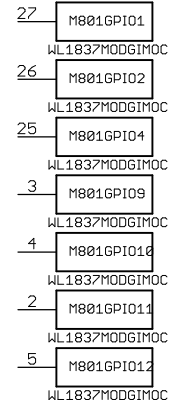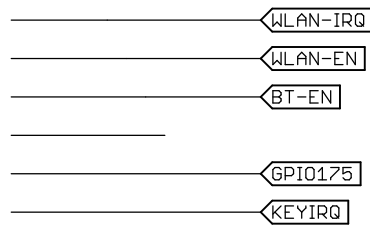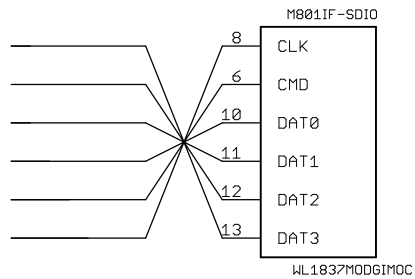secondary (on the side of GTA04)
could be 5.8GHz as well




WLAN & Bluetooth & FM

TITLE: GTA04b7-jr-first-beautify

Document Number:

REV:
v2b

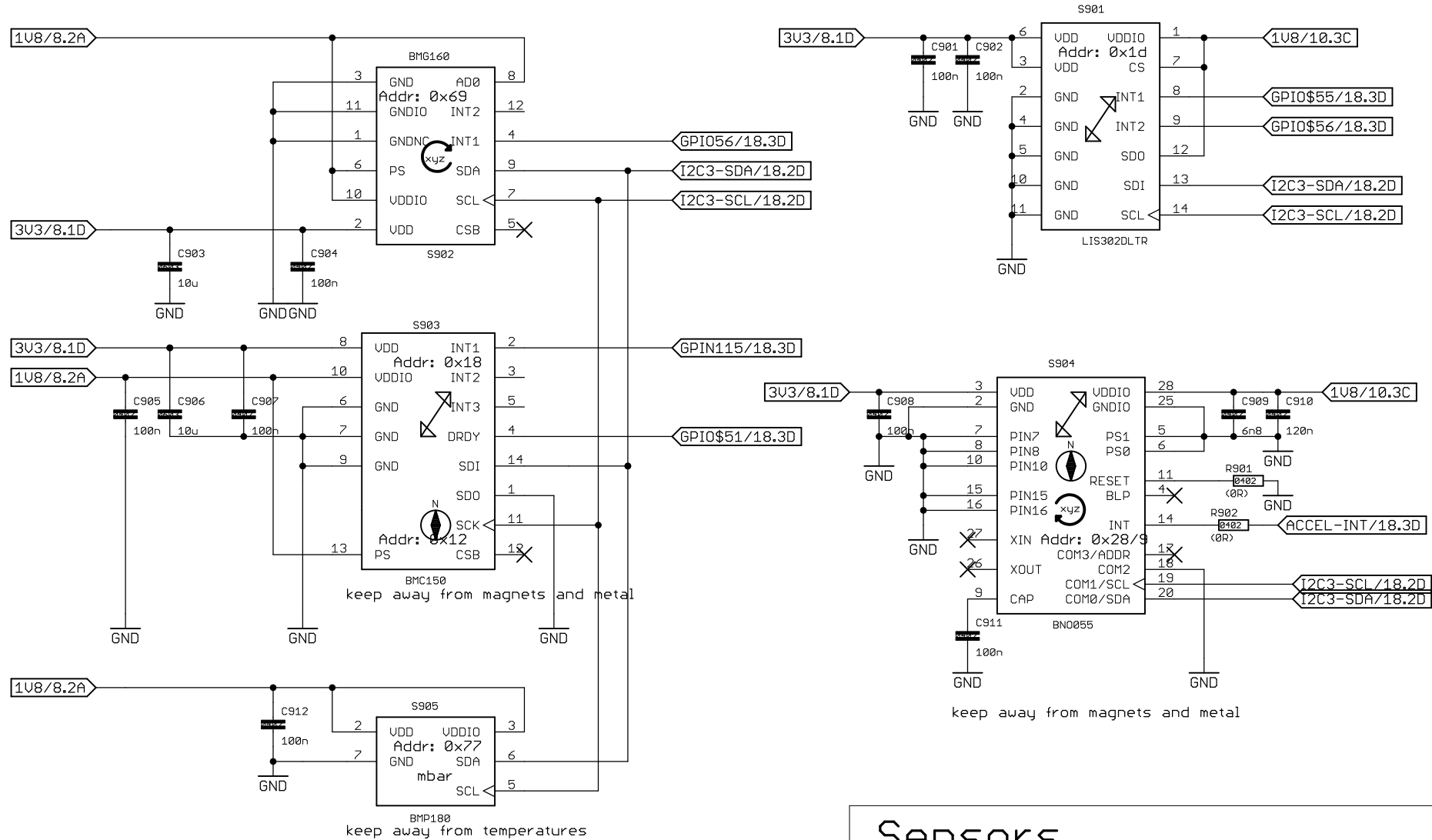

Sensors


TITLE: GTA04b7-jr-first-beautify


Document Number:


REU:
v2b

Date: 09.09.15 02:12


Sheet: 9/35

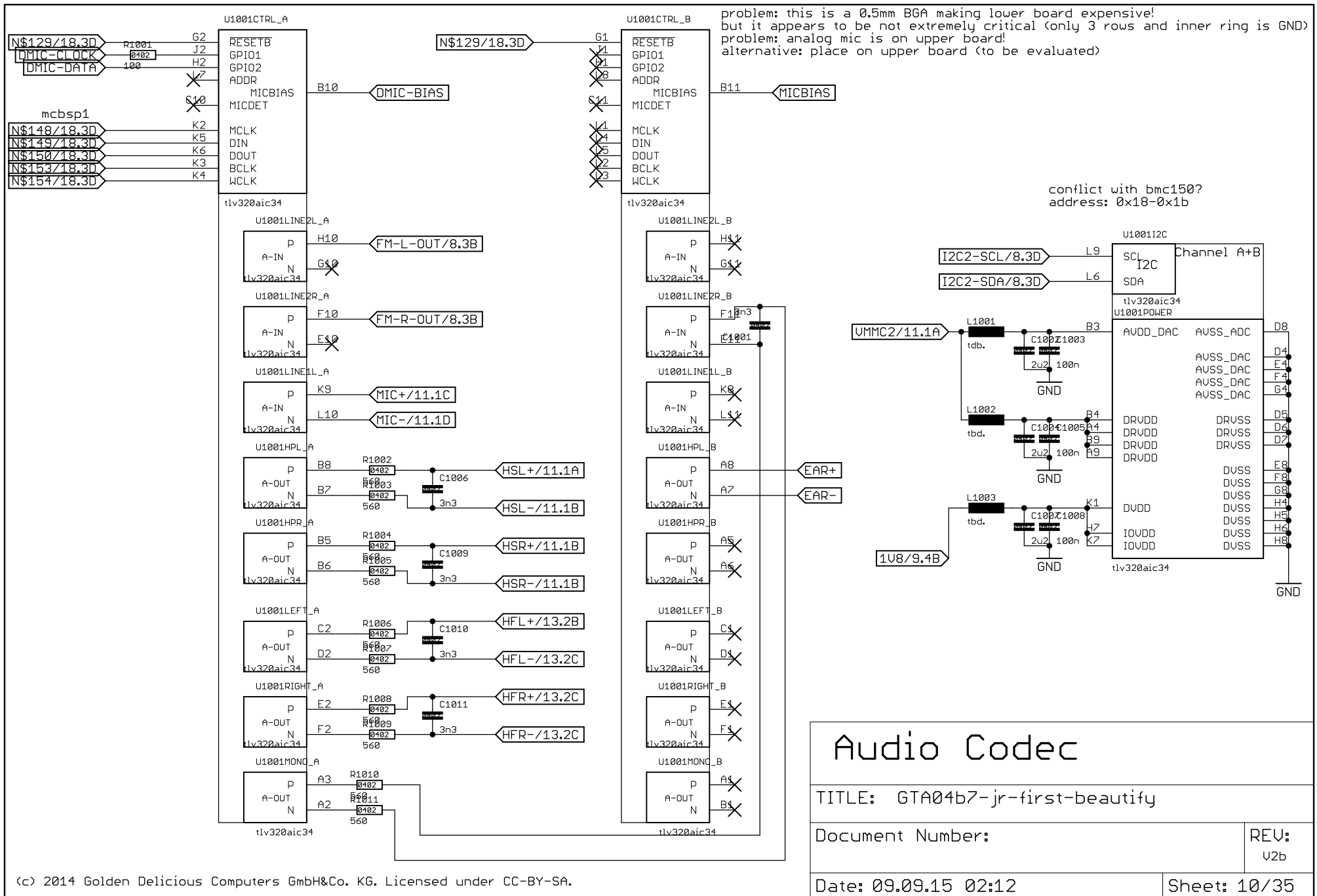

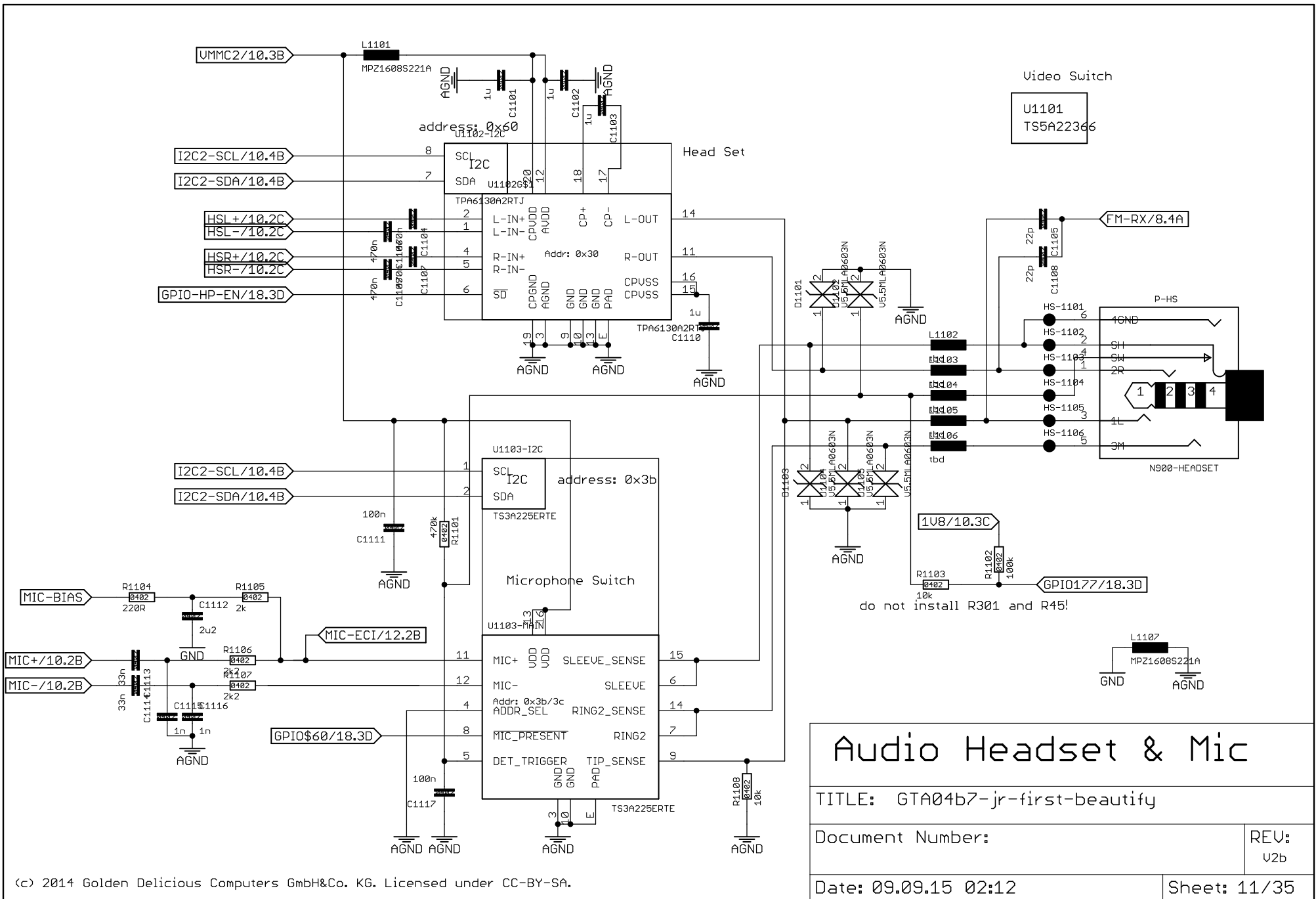

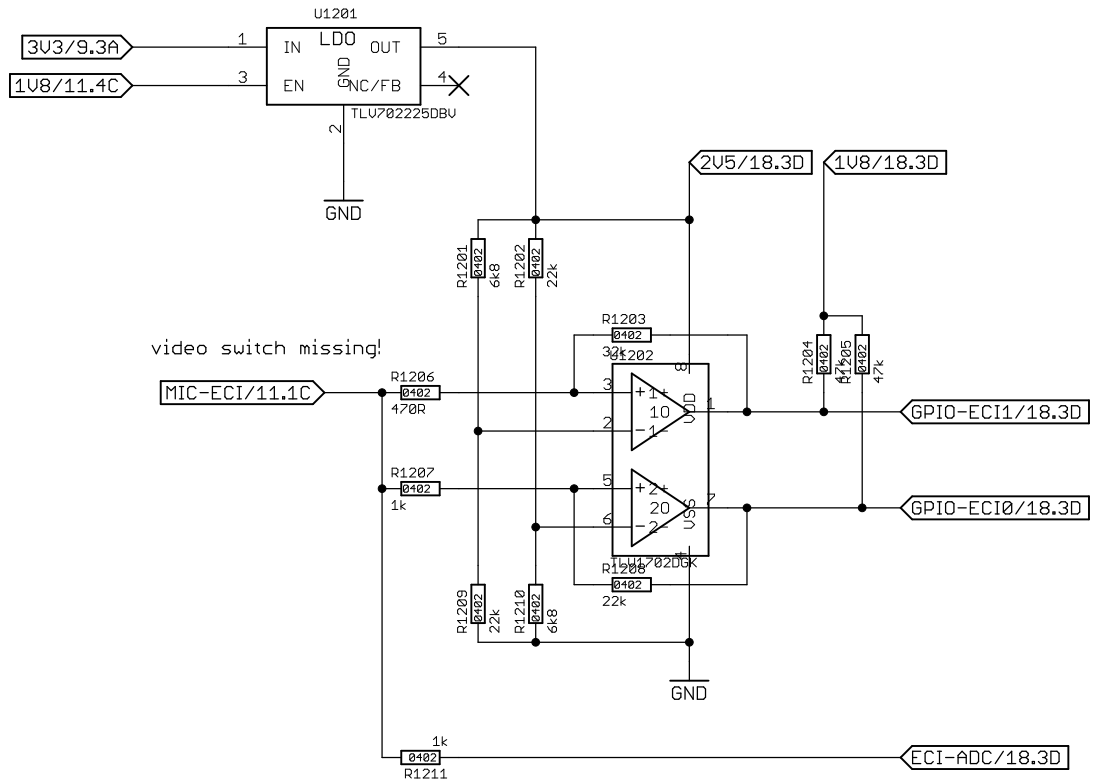

<h1>ECI</h1>	
TITLE: GTA04b7-jr-first-beautify	
Document Number:	REV: v2b
Date: 09.09.15 02:12	Sheet: 12/35

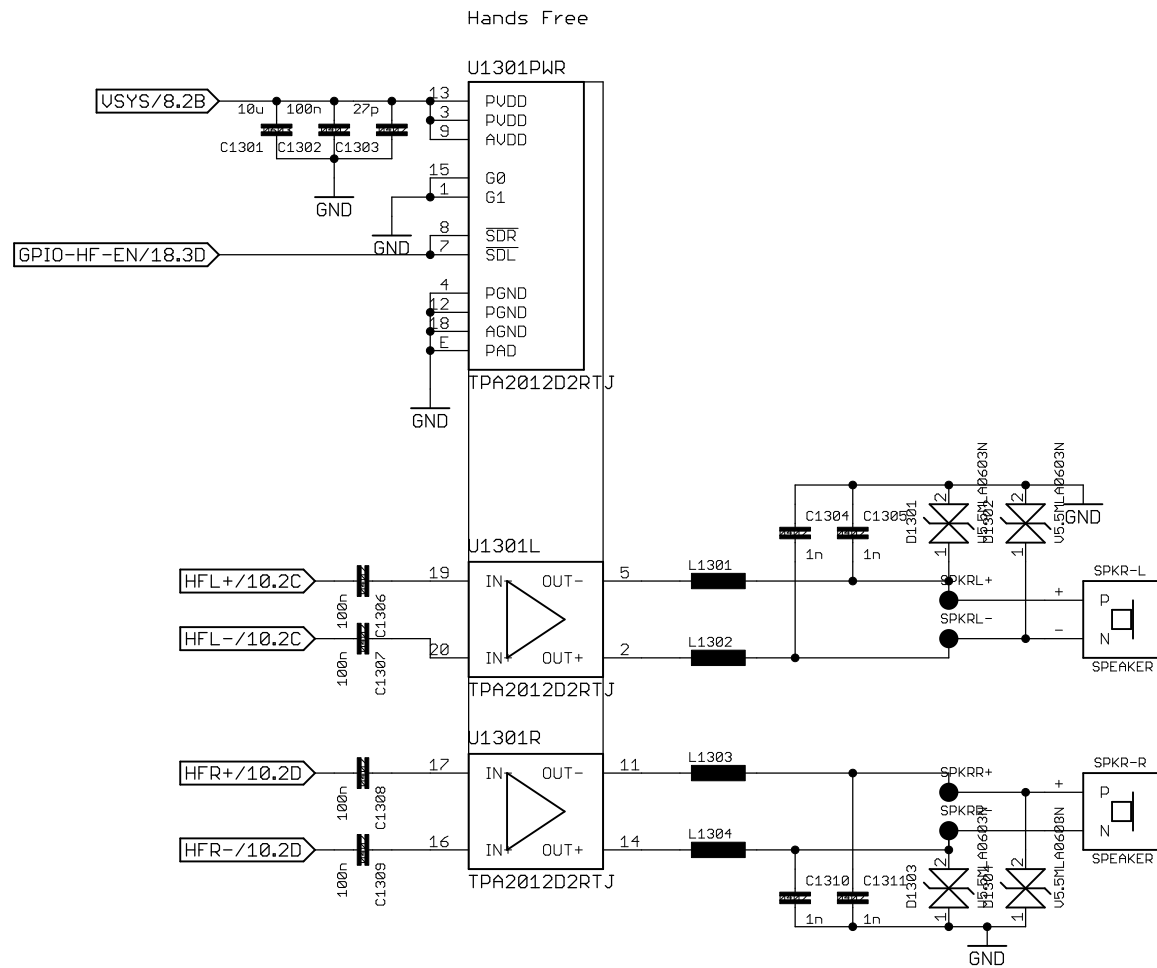

Audio Handsfree





TITLE: GTA04b7-jr-first-beautify

Document Number:


REU:
v2b

Date: 09.09.15 02:12

Sheet: 13/35

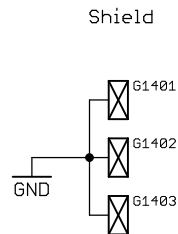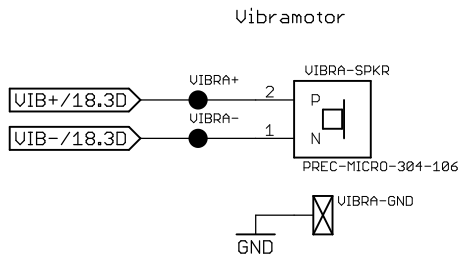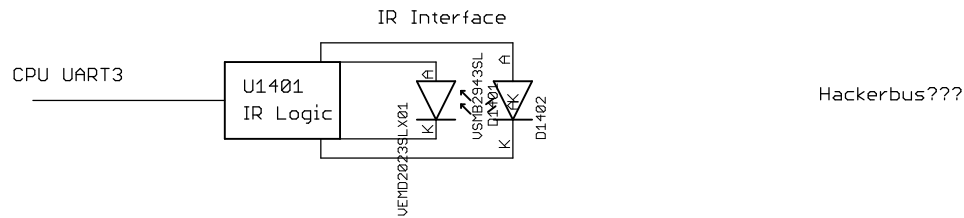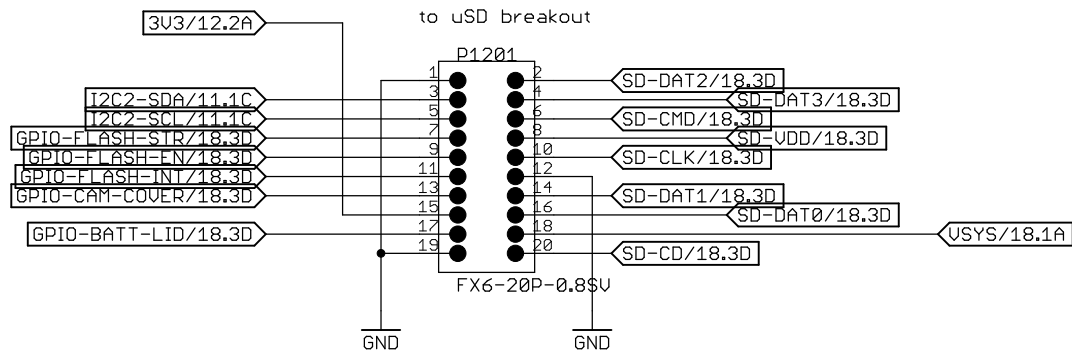

<h1>Misc (lower)</h1>	
TITLE: GTA04b7-jr-first-beautify	
Document Number:	REU: v2b
Date: 09.09.15 02:12	Sheet: 14/35

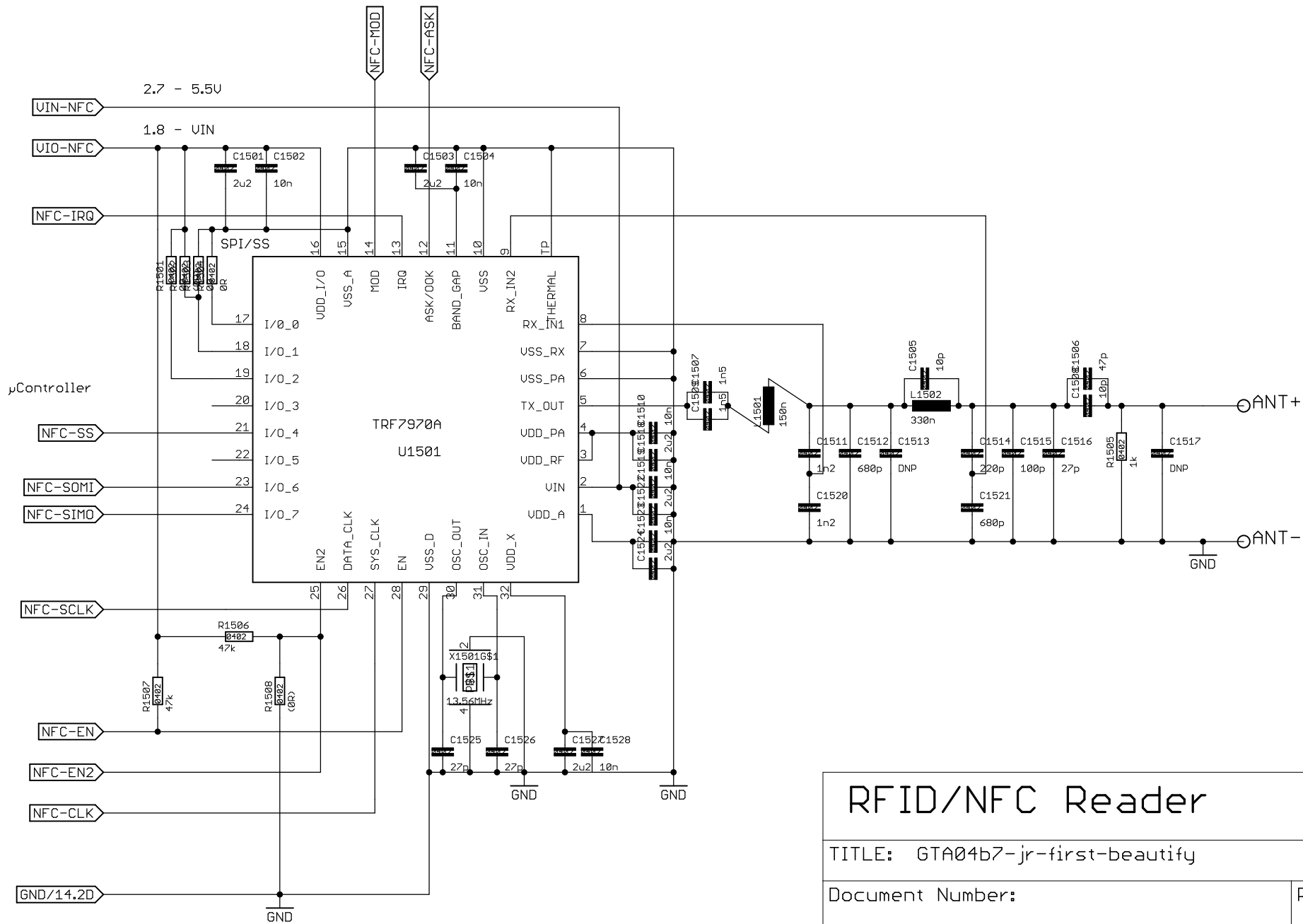

<h1>RFID/NFC Reader</h1>	
TITLE: GTA04b7-jr-first-beautify	
Document Number:	REU: v2b
Date: 09.09.15 02:12	Sheet: 15/35

Hackerbus

TITLE: GTA04b7-jr-first-beautify

Document Number:

REU:
v2b

Date: 09.09.15 02:12

Sheet: 16/35

Infrared

TITLE: GTA04b7-jr-first-beautify


Document Number:

REV:
v2b


Date: 09.09.15 02:12

Sheet: 17/35

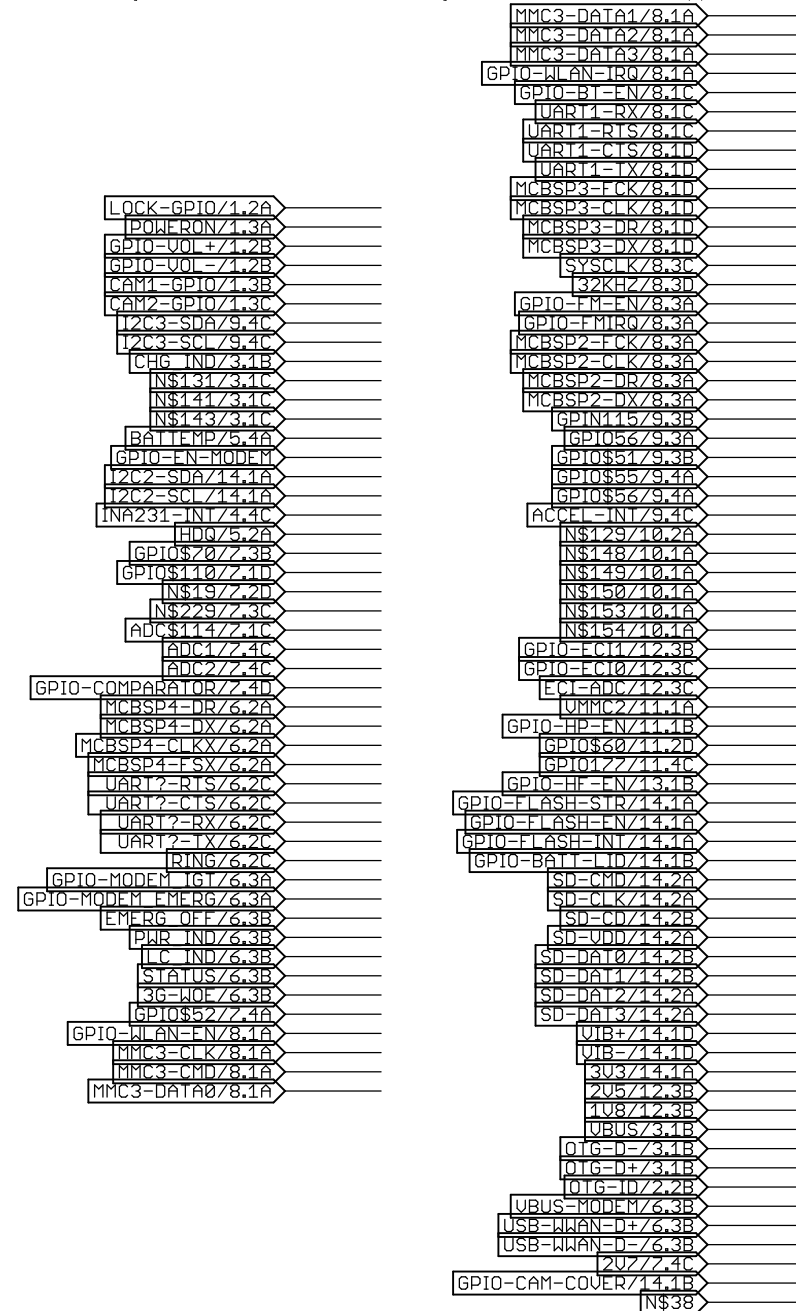ca. 130 signals (to be counted exactly after definition of upper/lower split)



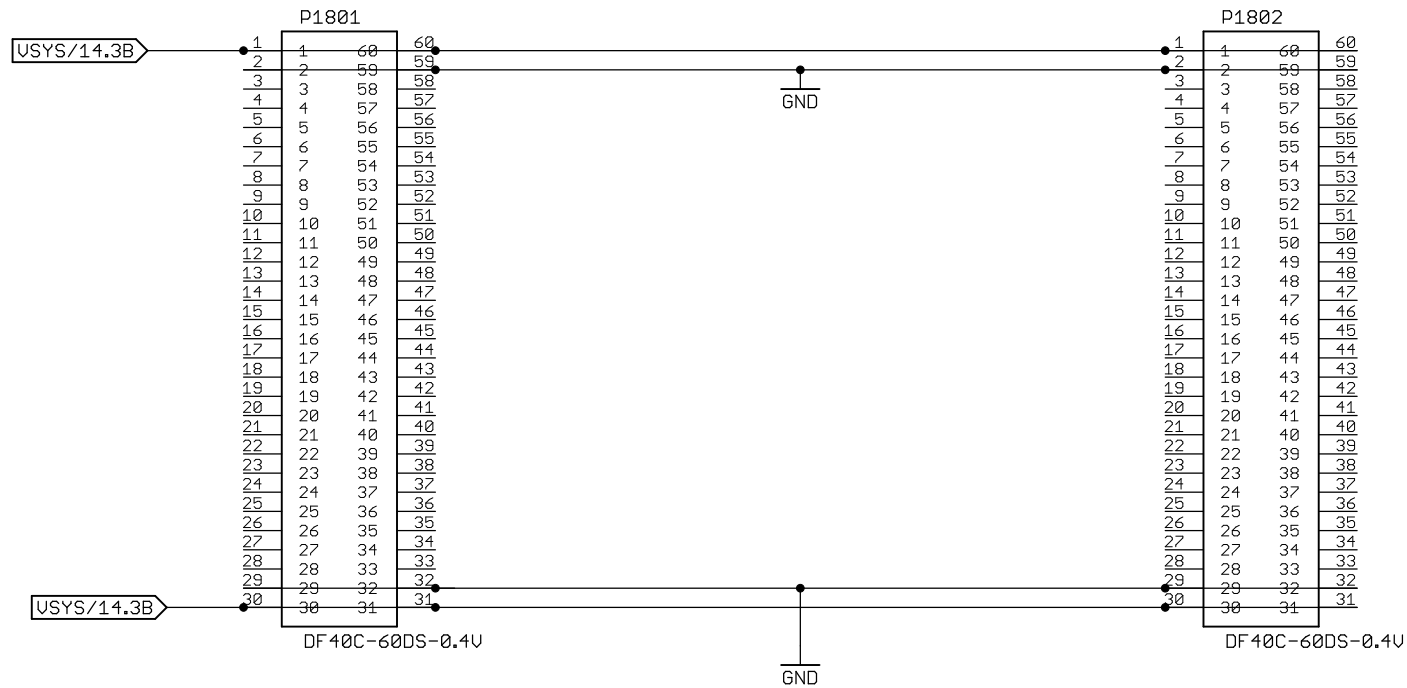Pin assignment must be optimized for final component placement
 we might have to switch to 80 or 100 pin connectors



B2B to upper board

TITLE: GTA04b7-jr-first-beautify



Document Number:

REV:
v2b

Date: 09.09.15 02:12

Sheet: 18/35

to be adjusted to lower board connector

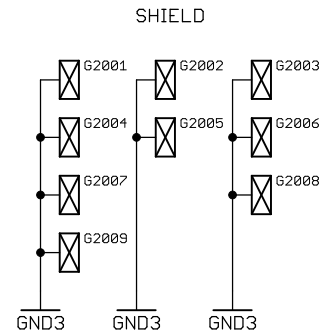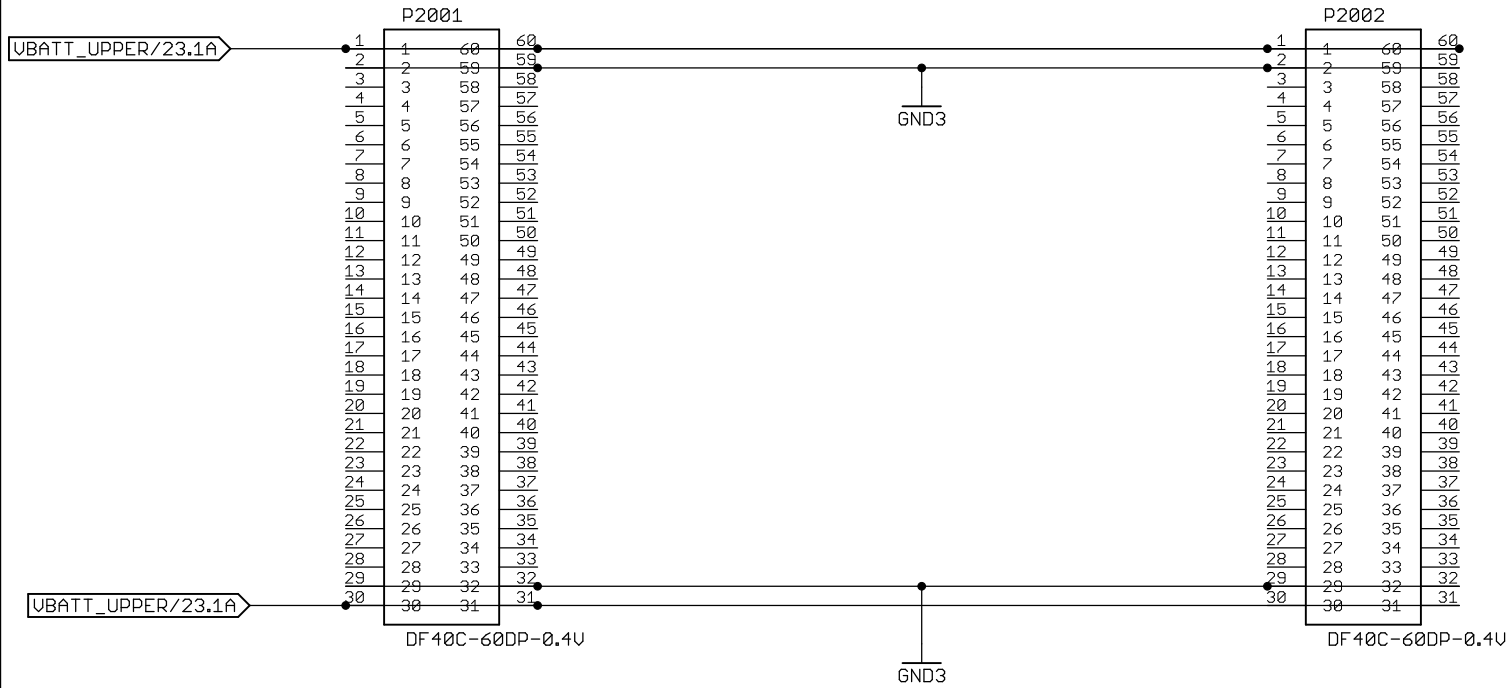

B2B to lower board

TITLE: GTA04b7-jr-first-beautify

Document Number:

REV:
v2b



Date: 09.09.15 02:12

Sheet: 20/35

needs final tuning (which button on which position)
 VOL+ and VOL- could drive FETs sitting in the matrix



1V8-CPU/22.1A

RESET_UPPER

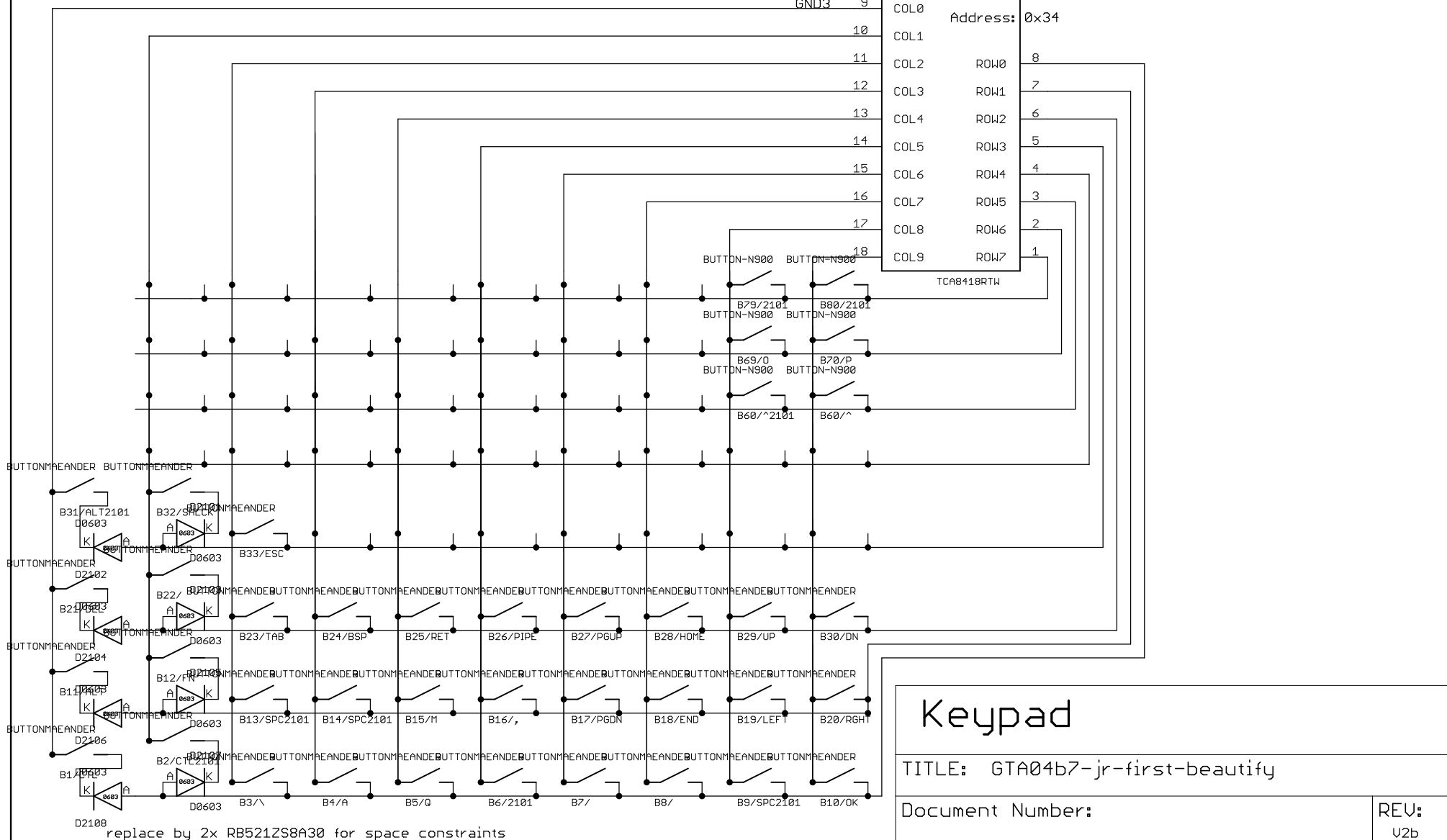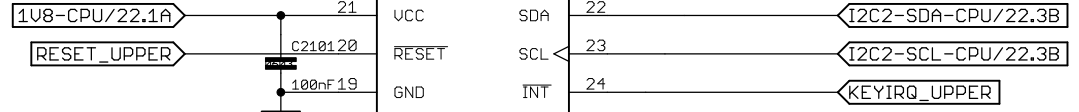

Keypad

TITLE: GTA04b7-jr-first-beautify	
Document Number:	REV: U2b
Date: 09.09.15 02:12	Sheet: 21/35

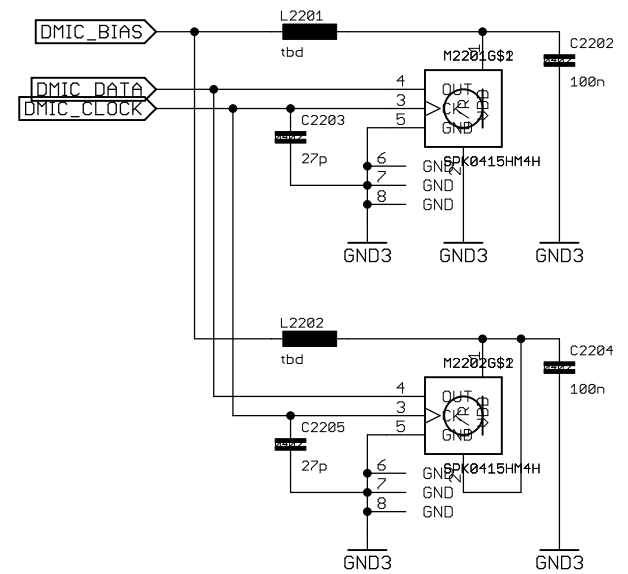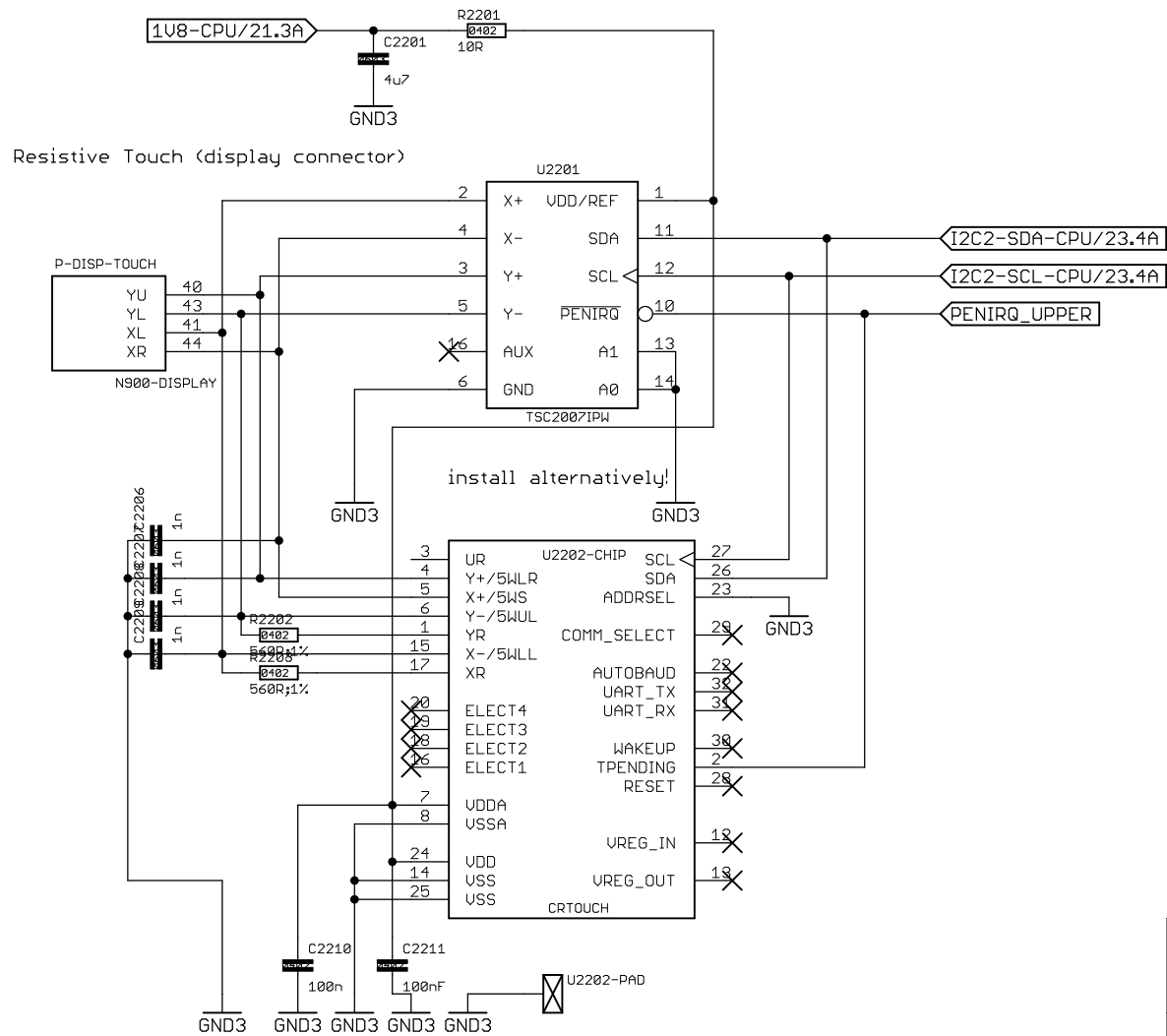

Display-Peripherals


TITLE: GTA04b7-jr-first-beautify

Document Number:

REV:
v2b

Date: 09.09.15 02:12





Sheet: 22/35

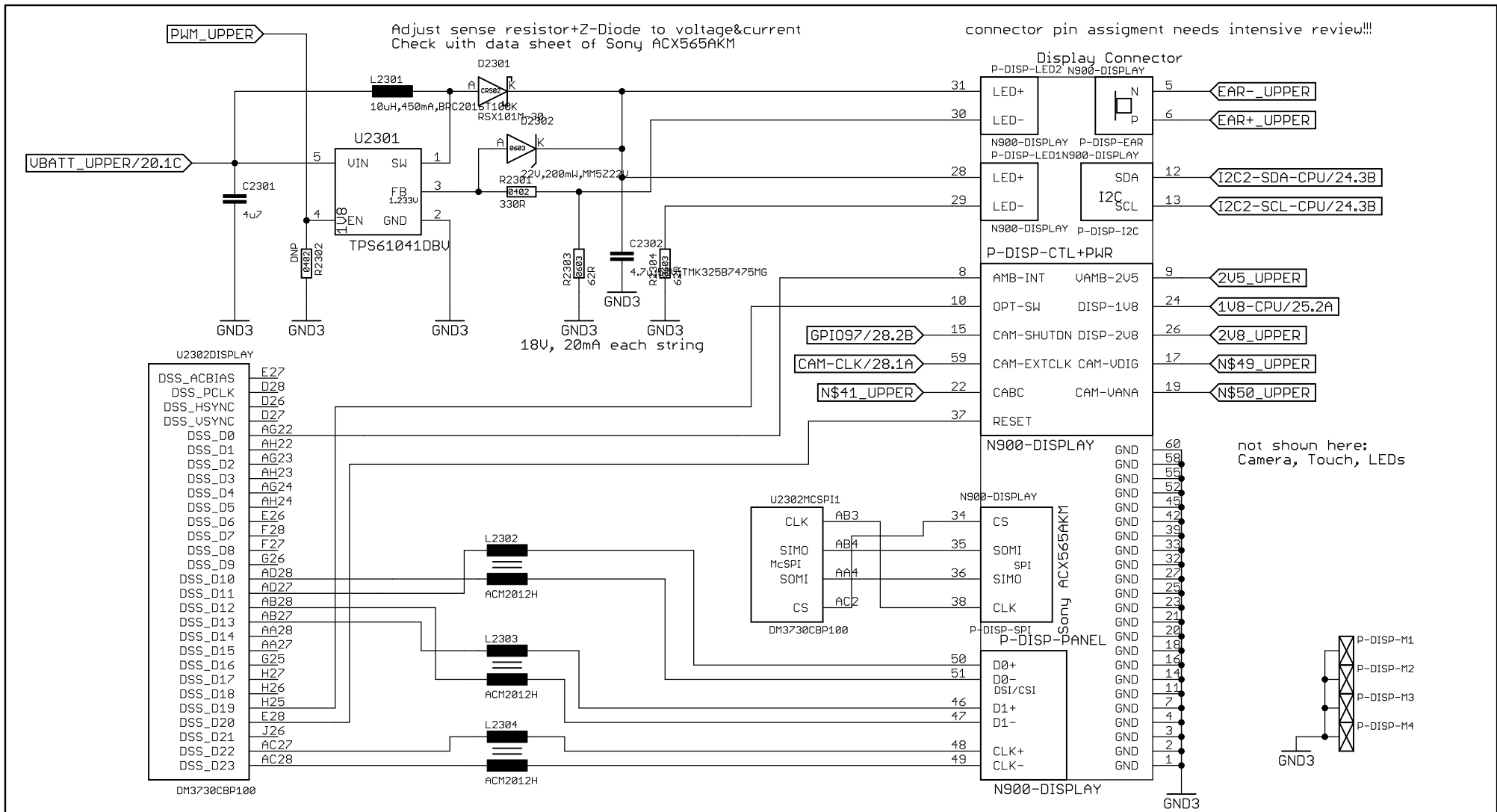

Display-Panel&Power

TITLE: GTA04b7-jr-first-beautify	
Document Number:	REV: v2b
Date: 09.09.15 02:12	Sheet: 23/35

INCOMPLETE in U2

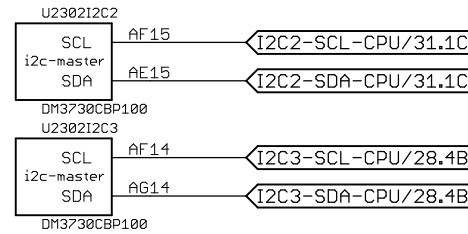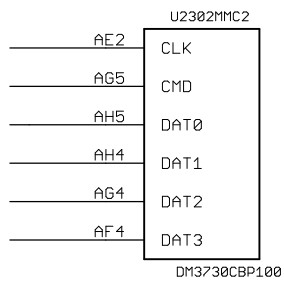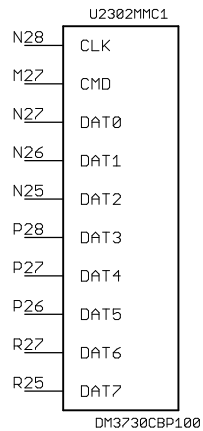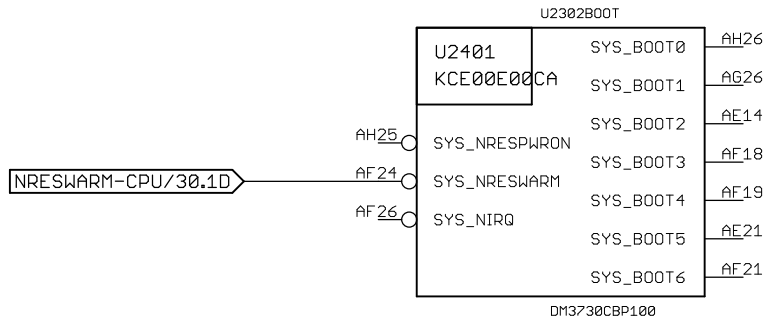

CPU + PoP RAM/NAND

TITLE: GTA04b7-jr-first-beautify


Document Number:

REV:
v2b

Date: 09.09.15 02:12

Sheet: 24/35

INCOMPLETE in U2

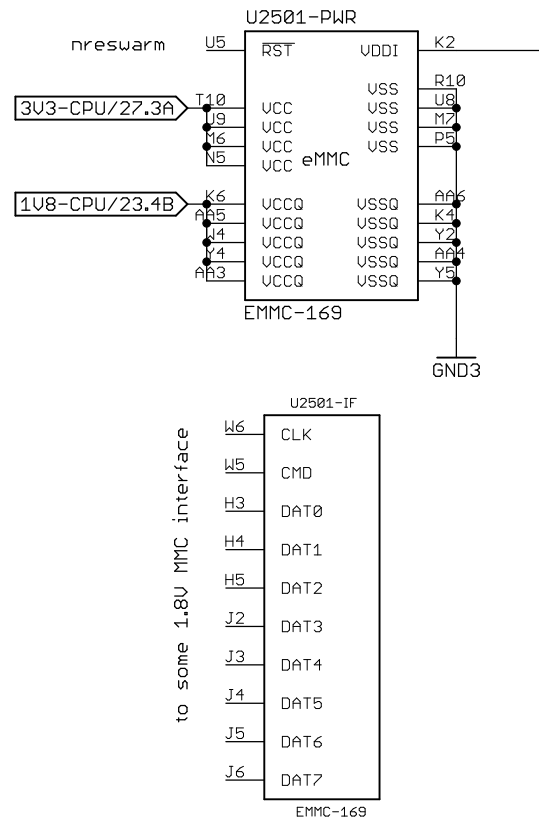

eMMC


TITLE: GTA04b7-jr-first-beautify


Document Number:

REU:
v2b

Date: 09.09.15 02:12

Sheet: 25/35

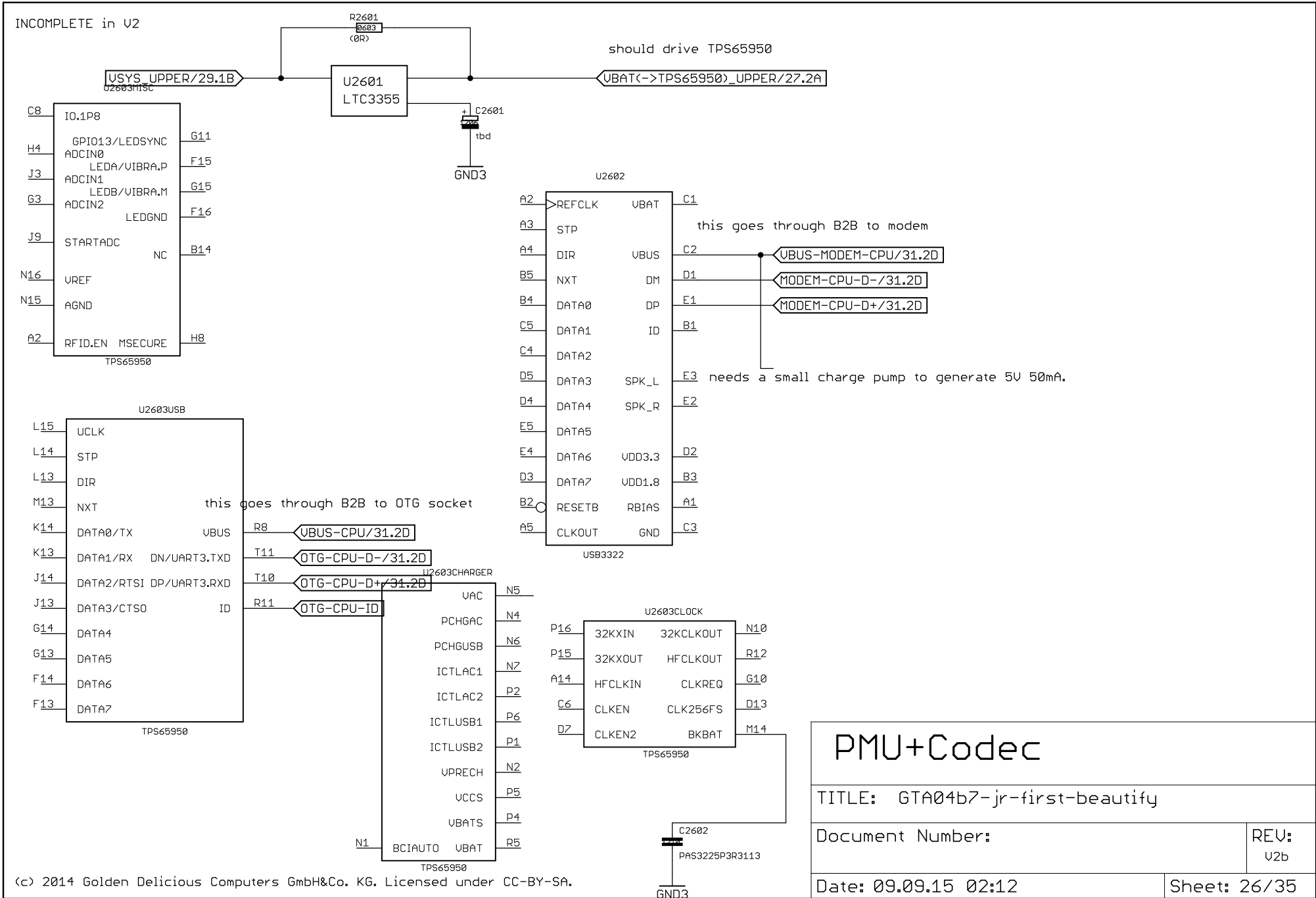

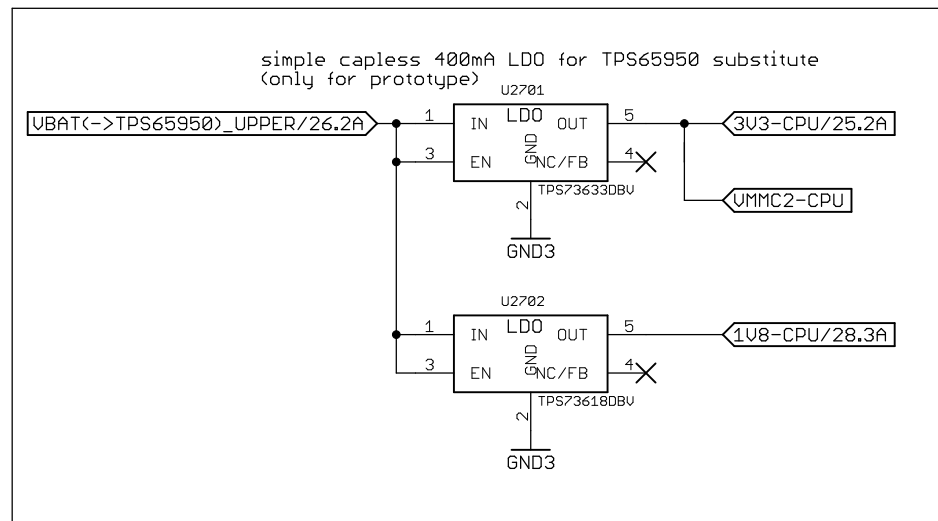

BB-XM Dummy (TWL4030)

TITLE: GTA04b7-jr-first-beautify


Document Number:

REU:
v2b

Date: 09.09.15 02:12


Sheet: 27/35

INCOMPLETE in U2

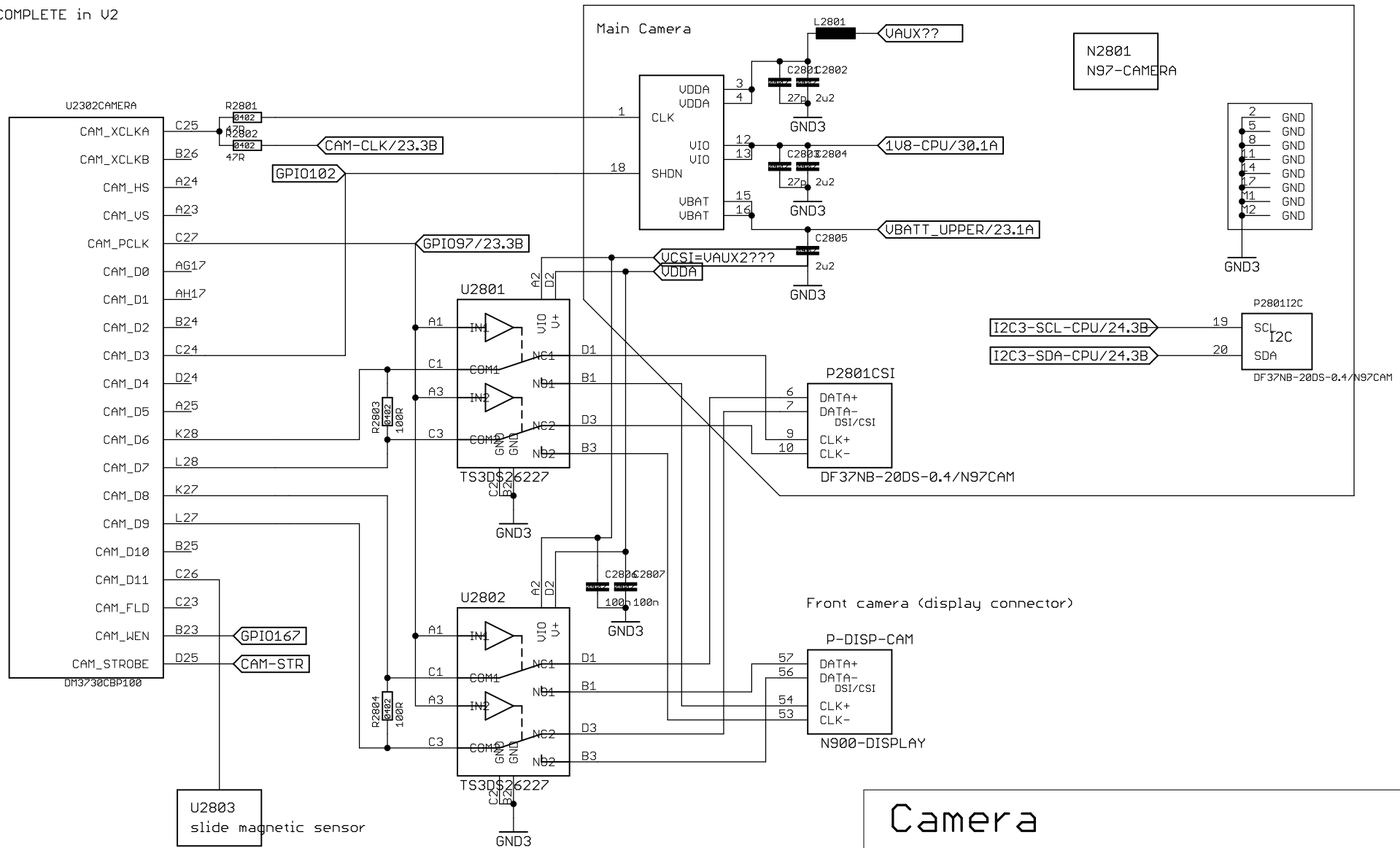


<h1>Camera</h1>	
TITLE: GTA04b7-jr-first-beautify	
Document Number:	REV: v2b
Date: 09.09.15 02:12	Sheet: 28/35

AUX and Display LEDs

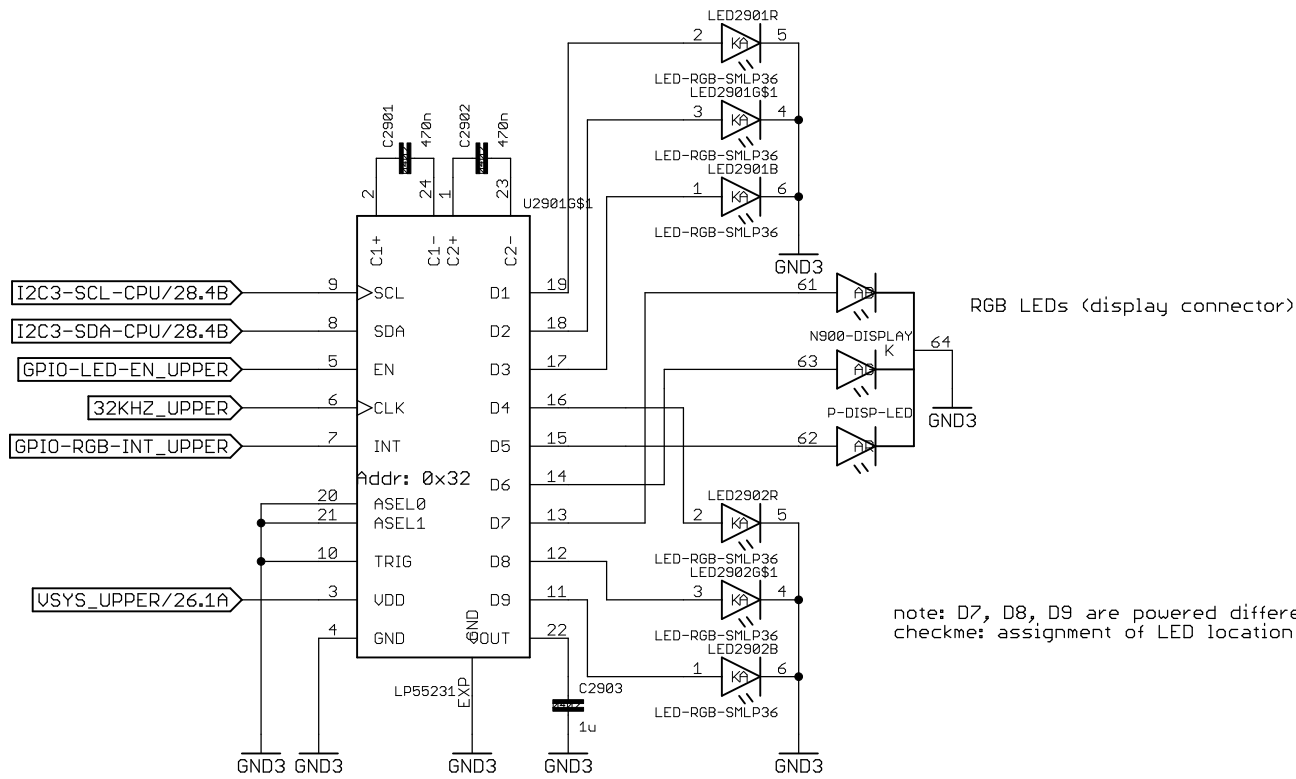

note: D7, D8, D9 are powered differently!
 checkme: assignment of LED location to output number

<h1>LEDs</h1>	
TITLE: GTA04b7-jr-first-beautify	
Document Number:	REU: v2b
Date: 09.09.15 02:12	Sheet: 29/35

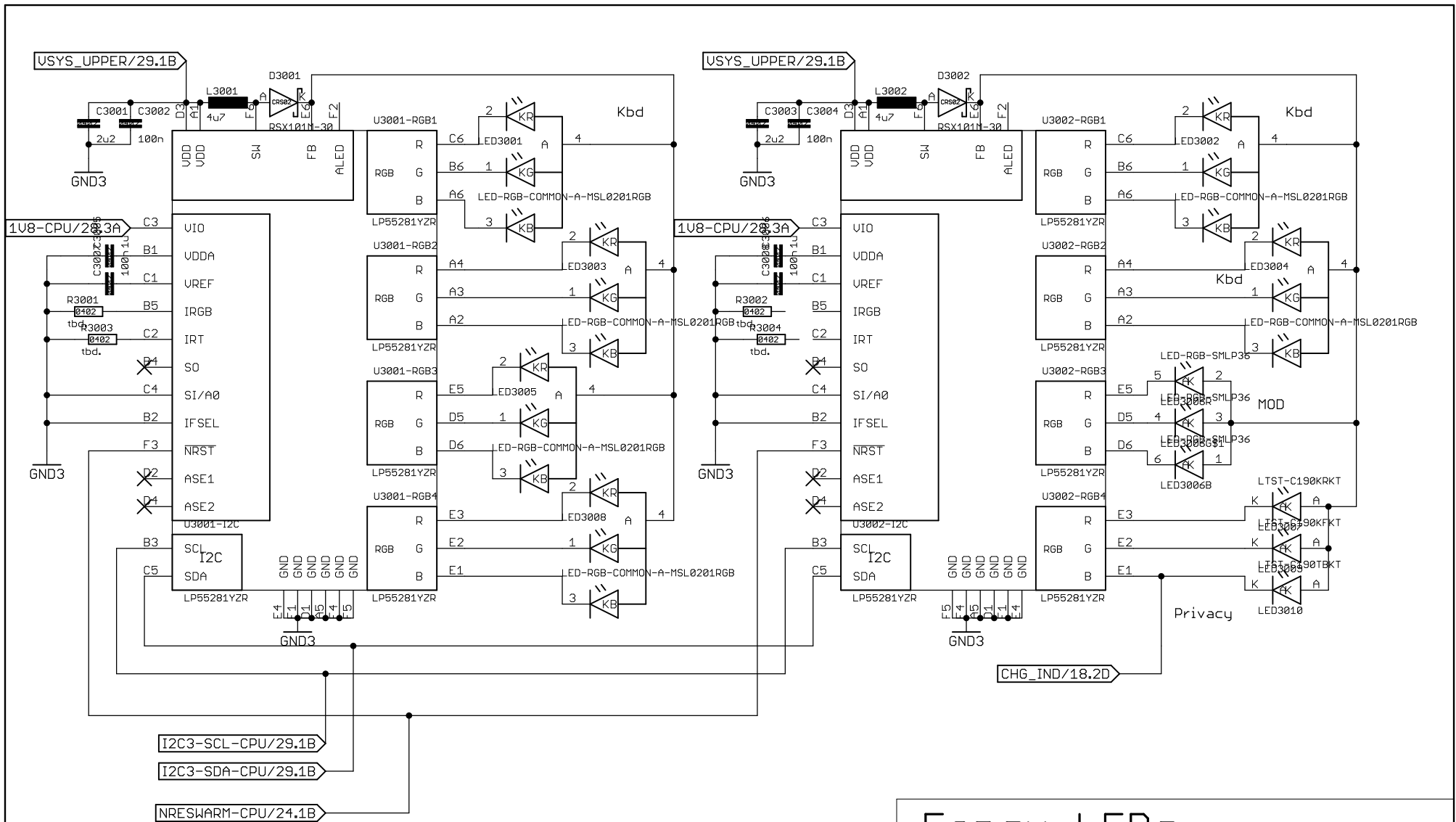


<h1>Fancy LEDs</h1>	
TITLE: GTA04b7-jr-first-beautify	
Document Number:	REU: v2b
Date: 09.09.15 02:12	Sheet: 30/35


These connectors allow to "emulate" the DM3730 by connecting a BB-XM

INCOMPLETE
prototype only

connect to respective CPU-pads

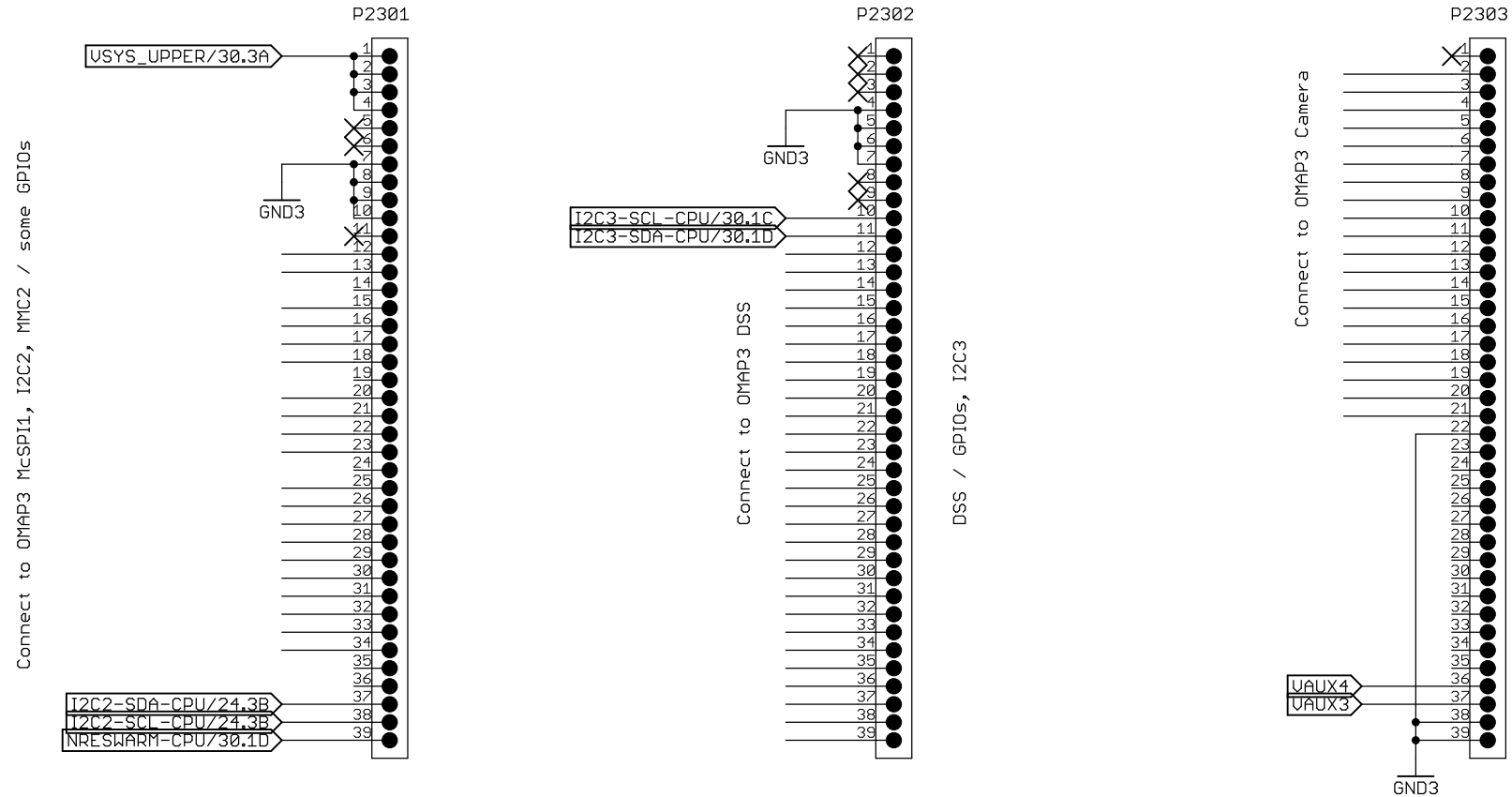

connect to BB
by some Micro-USB cable

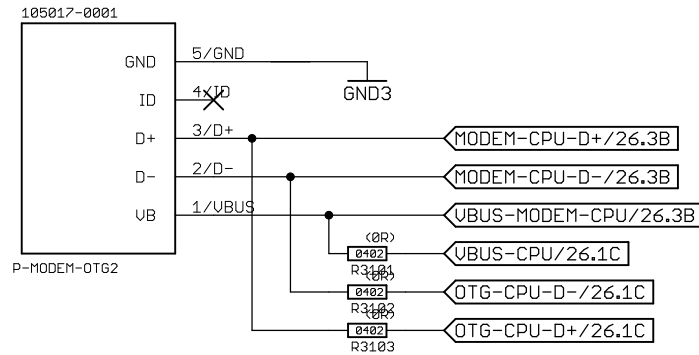

Connector to BB


TITLE: GTA04b7-jr-first-beautify

Document Number:


REV:
v2b

Date: 09.09.15 02:12

Sheet: 31/35

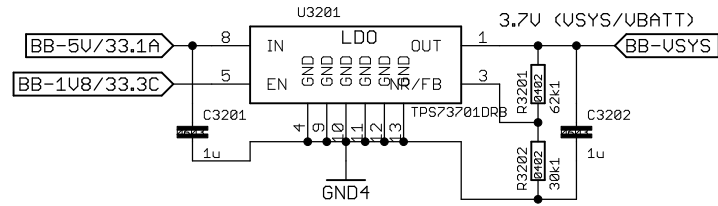

Ersetzen durch 2A buck converter

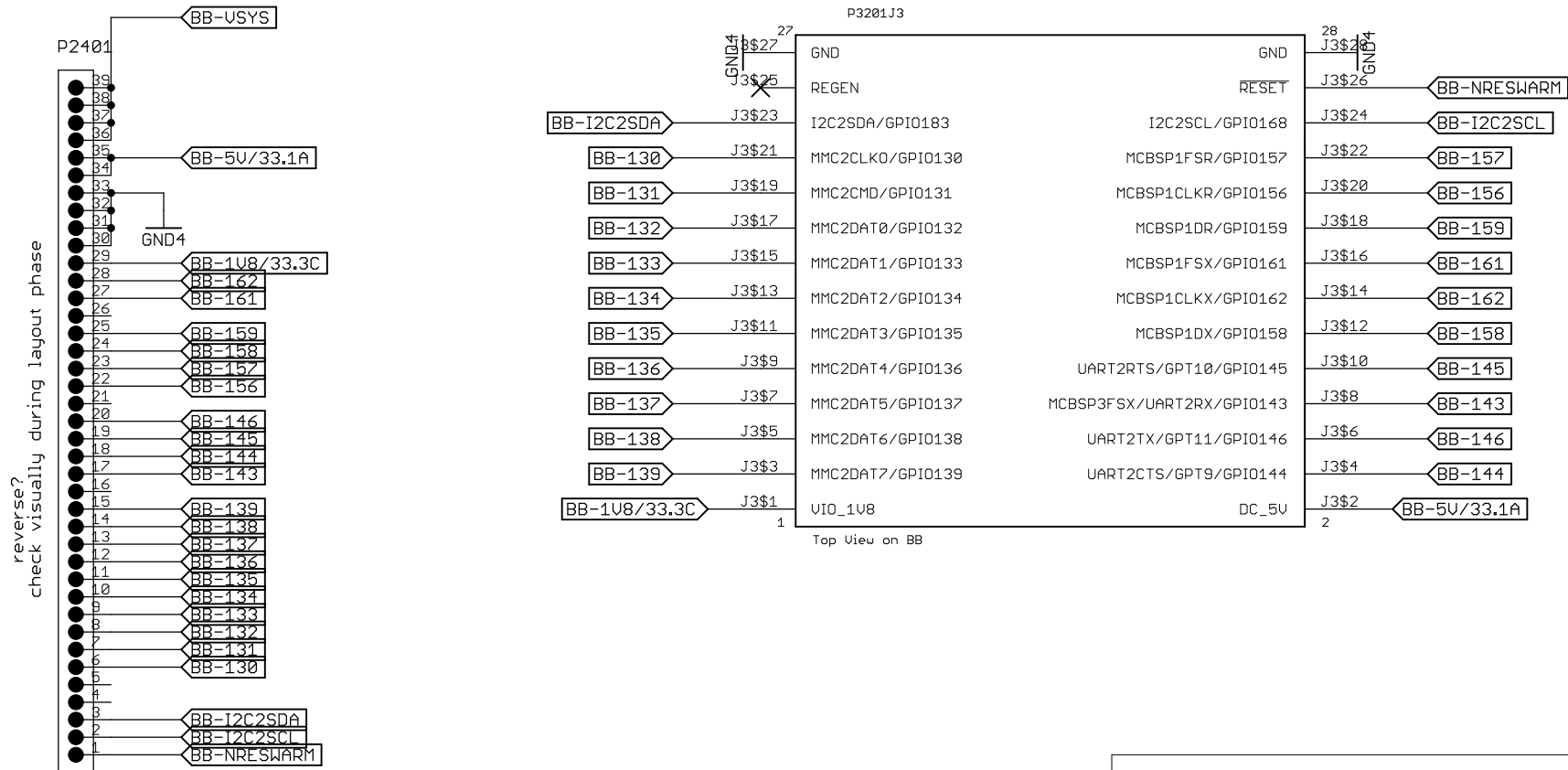




BB-XM Adapter (CPU)

TITLE: GTA04b7-jr-first-beautify

Document Number: REU:
v2b

Date: 09.09.15 02:12 Sheet: 32/35

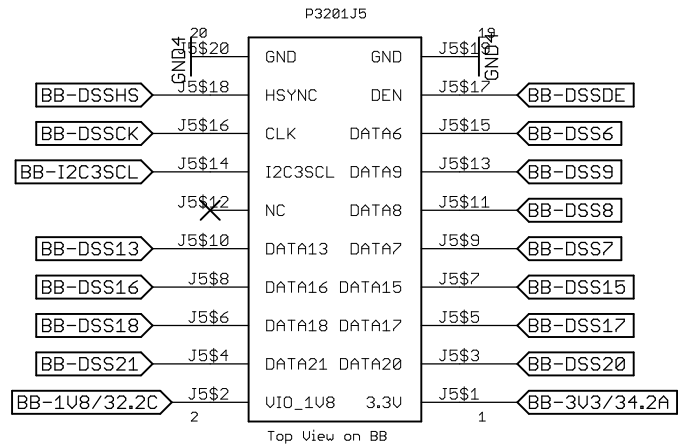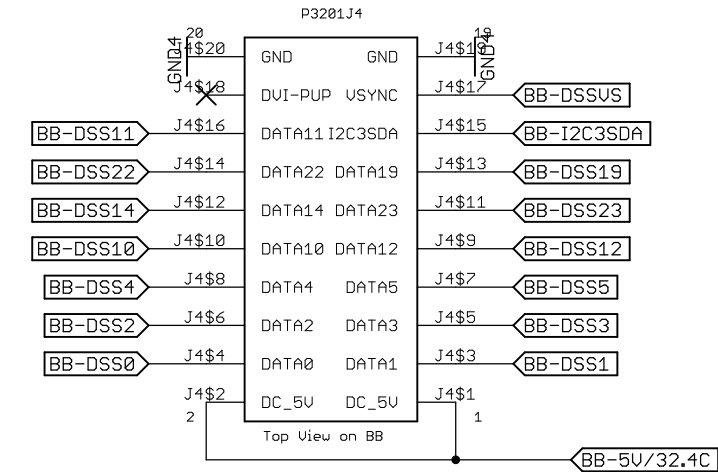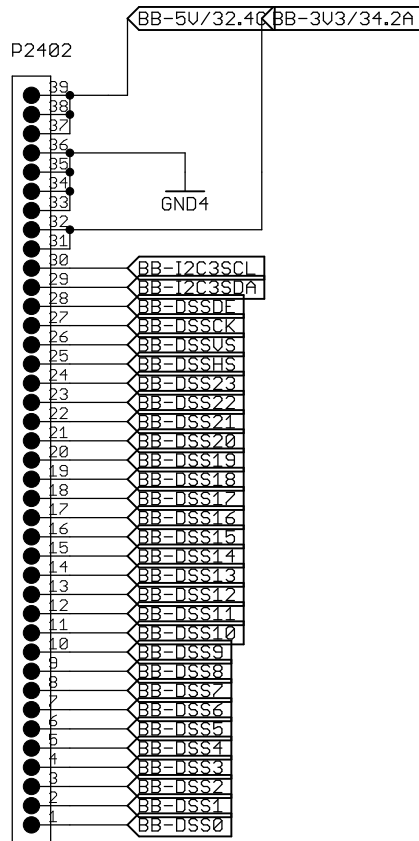reverse?
check visually during layout phase



BB-XM Adapter (DISP)


TITLE: GTA04b7-jr-first-beautify

Document Number:

REV:
v2b

Date: 09.09.15 02:12


Sheet: 33/35

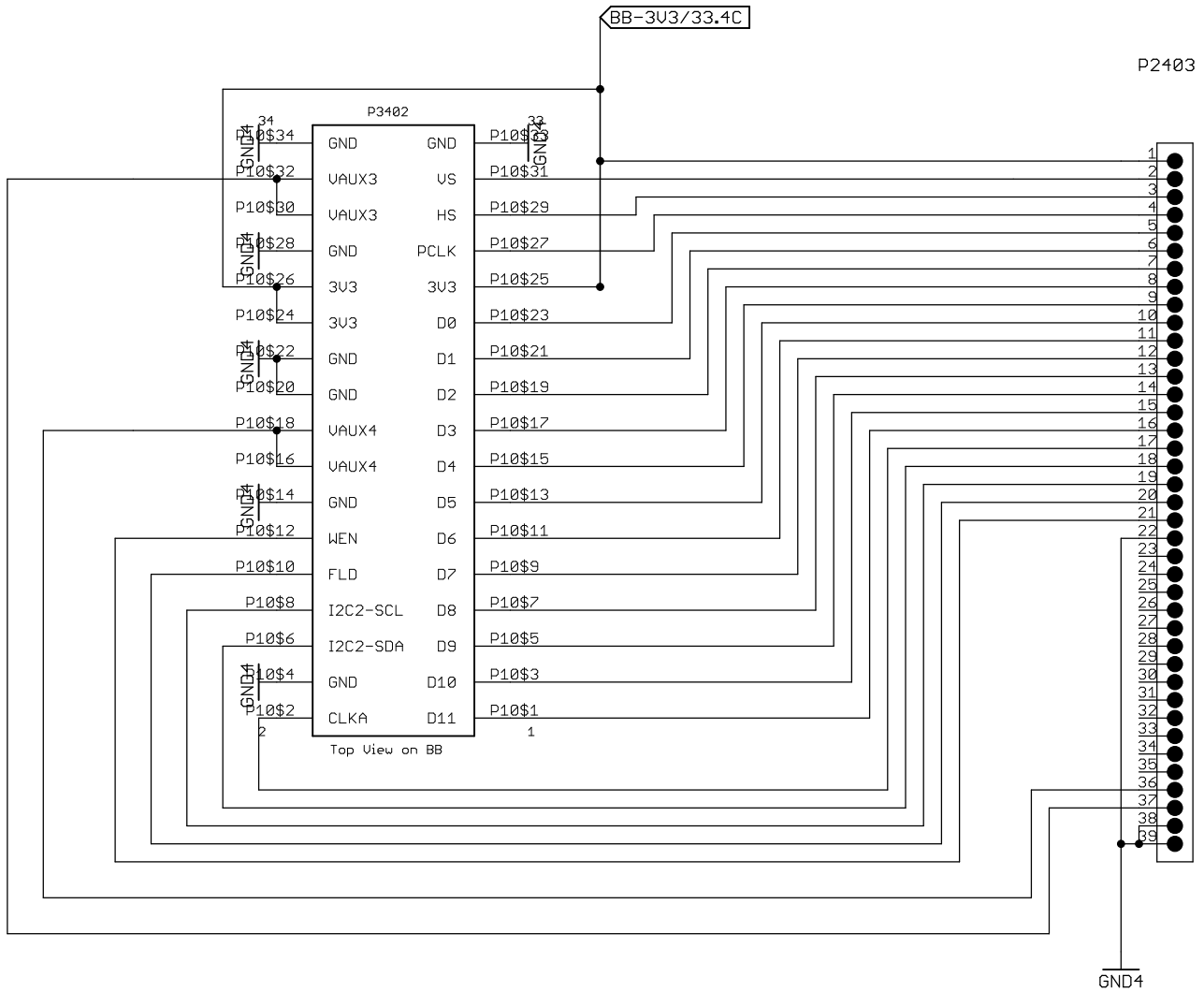

reverse?
check visually during layout phase

<h1>BB-XM Adapter (CAM)</h1>	
TITLE: GTA04b7-jr-first-beautify	
Document Number:	REU: v2b
Date: 09.09.15 02:12	Sheet: 34/35

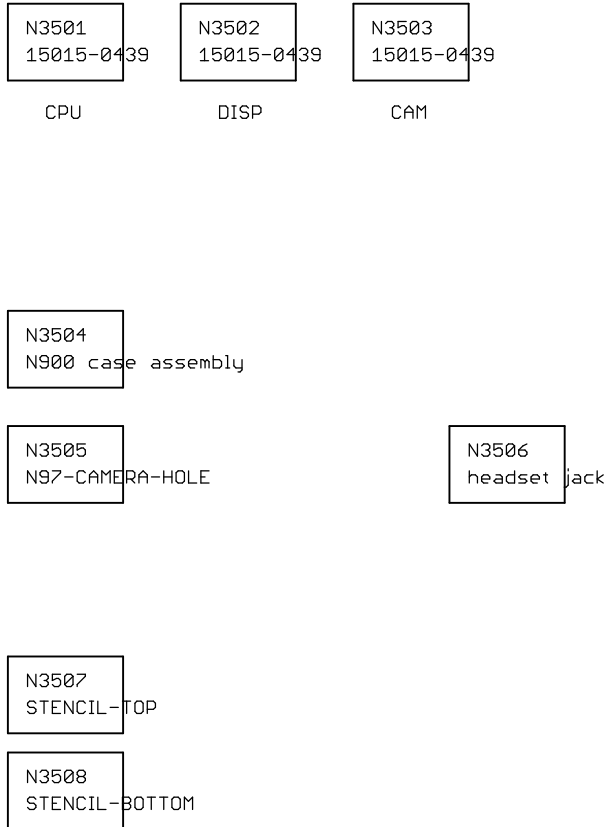Molex Jumper cables to connect BB-XM-Adapter to Uppwer board



No-Solder Components

TITLE: GTA04b7-jr-first-beautify

Document Number:

REU:
v2b

Date: 09.09.15 02:12

Sheet: 35/35